

Subject Name Electrical Engineering

| Unit No | Unit Name           | Syllabus Topics                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  | Lecture No                                                                   |
|---------|---------------------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------|
| 1       | Electrical Machines | DC machines principle & Construction<br>DC Generator-e.m.f equation, types, applications<br>DC Motor- Working, torque equation, back e.m.f<br>DC Motor- Types, characteristics of series and shunt motor, applications<br>Three phase induction motor: Construction and working<br>Sels, Sep-torque characteristics of three phase induction motor<br>Single phase induction motor - Working & starting<br>Synchronous motor - starting and working<br>LT Switchgear: Switch Fuse Unit (SFU), MCCB<br>LT Switchgear: DCCB, MCCB, ACB<br>Types of Wires and Cables, Fundamental of earthing & Lightning protection<br>Types of Batteries, Bus bar | 27<br>28<br>29<br>30<br>31<br>32, 33<br>34, 35<br>36<br>37<br>38<br>39<br>40 |


|                      |                        |
|----------------------|------------------------|
| Signature            |                        |
| Name of Subject Head | Mr. Ashok Kumar Rajput |

## Unit - 2 STEADY STATE ANALYSIS OF AC CIRCUIT


ALTERNATING QUANTITY (AC)  
An alternating quantity is that which acts in alternating direction & whose magnitude undergoes a definite cycle of change in definite intervals of time.

In India, the frequency of a.c is 50 Hz.

Sine wave

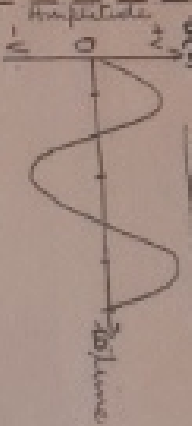


Complex wave

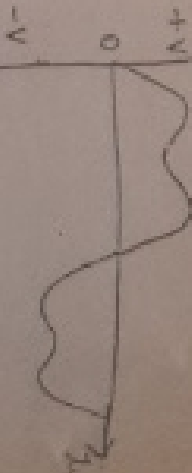

Triangular wave




Square wave

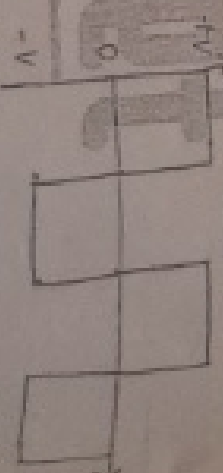
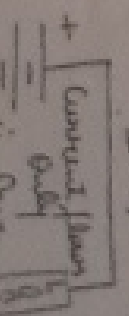
## DIRECT CURRENT (DC)

When the electric charge inside the conductor flows in one direction, then such type of current is called direct current. The magnitude of direct current always remains constant and the direction of current is unidirectional. It is used in cell phones, electric vehicles, electronic equipment etc.



1) Waveform: The graph of instantaneous values of an alternating quantity plotted against time is called its waveform.

2) Instantaneous value: The value of an alternating quantity at a particular instant is called its instantaneous value.

3) Cycle: One complete set of positive & negative values & zero values of an alternating quantity is called a cycle.

Sometimes, a cycle is specified in terms of angular measure. In that case, one complete cycle is said to spread over  $360^\circ$  or  $2\pi$  radians.

4) Time period: Time taken by an alternating quantity to complete one cycle is called its time period ( $T$ ).

5) Frequency: No. of cycles per second is called frequency of an alternating quantity. Its unit is Hertz (Hz).

$$f = \frac{1}{T}$$

sec<sup>-1</sup> or Hertz

6) Amplitude: Maximum positive or negative value, or an alternating quantity is known as its amplitude. Eg.  $i = 150 \sin \omega t$

Amplitude is  $i_0 = 150 \text{ Amp}$

7) Angular frequency: It is the frequency expressed in radians per second.


One cycle is of alternating quantity corresponds to  $2\pi$  radians, the angular frequency is  $\omega = 2\pi f$  rad/sec

8) Phase: Phase of an alternating quantity is the fraction of time period which elapses that a quantity must elapse from time zero to  $\omega t$ .

$$e = E_m \sin(\omega t + 90^\circ)$$

1) Phase difference: It is defined as angular displacement between two sinusoidal wave functions.

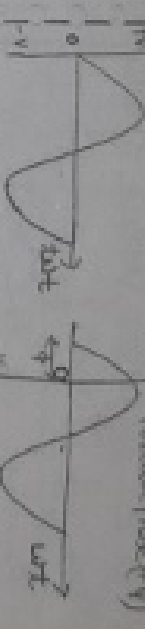2) Phase difference: It is defined as angular displacement between two sinusoidal wave functions.



$$v(t) = V_m \sin \omega t$$

$$v(t) = V_m \sin(\omega t + \phi)$$

$$v(t) = V_m \sin(\omega t - \phi)$$

3) Average value: The average value of an alternating quantity is expressed by that steady current which transfers across any circuit the same amount of energy as the alternating current during the same time.

4) Average value: The average value of an alternating quantity is expressed by that steady current which transfers across any circuit the same amount of energy as the alternating current during the same time.

5) Average value: The average value of an alternating quantity is expressed by that steady current which transfers across any circuit the same amount of energy as the alternating current during the same time.

6) Average value: The average value of an alternating quantity is expressed by that steady current which transfers across any circuit the same amount of energy as the alternating current during the same time.

7) Average value: The average value of an alternating quantity is expressed by that steady current which transfers across any circuit the same amount of energy as the alternating current during the same time.

$$V_{avg} = \frac{1}{T} \int_0^T f(t) \cdot dt$$

R.M.S value :- It is defined as that steady current which when flows through a resistor of known resistance for a given period of time as a result the same quantity of heat is produced by an alternating current with flows through the same resistor for the same period of time is called R.M.S or effective value of alternating current.

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

Form factor :- It is defined as the ratio of R.M.S value to the Average value of an alternating waveform.

$$\text{Form factor } (K_f) = \frac{\text{R.M.S value}}{\text{Average value}}$$



$$K_f = \frac{V_{max}/\sqrt{2}}{V_{max}/\pi}$$

PEAK FACTOR OR CREST FACTOR OR AMPLITUDE FACTOR

It is the ratio of maximum value to the R.M.S value of an alternating wave. For sinusoidal wave of voltage, Peak factor is 1.4142.

$$\text{Peak factor} = \frac{\text{Maximum value}}{\text{R.M.S value}}$$

For sinusoidal waveform

$$\text{Peak factor } (K_p) = \frac{V_{max}}{V_{rms}}$$

$$K_p = \sqrt{2} = 1.414$$

Ques: An alternating voltage is given by  $v = 141.4 \sin 314t$  Find out :-

- (i) Frequency (ii) Instantaneous value when  $t = 3ms$
- (iii) Amplitude (iv) Time taken for the voltage to reach 100V for the first time after passing through zero value
- (v) Zero value (vi) max. positive value.
- (vi) rms value & average value

Ans: (i) 20, 17-18, 15-16

Sol:-

Given:-

$v = 141.4 \sin 314t$ , Compare it with

- (i)  $v = V_m \sin \omega t$
- (ii)  $\omega = 314 \text{ rad/sec}$
- (iii)  $2\pi f = 314$

$$f = \frac{50 \text{ Hz}}{2\pi}$$

- (iv) Put  $t = 3ms$  in the equation

$$v = 141.4 \sin (314 \times 0.003) = 114.4 \text{ Volt}$$

- (v) time taken from  $t = 0$  to reach 100V

$$100 = 141.4 \sin 314t$$

$$t = \frac{1}{314} \sin^{-1} \left( \frac{100}{141.4} \right) = (2.5 \text{ ms}) \quad \left\{ \text{Use radian mode in calculator} \right\}$$

- (vi) From max. positive value

$$v = 141.4 \sin (314t + \pi/2)$$

$$v = 141.4 \cos 314t$$

$$100 = 141.4 \cos 314t$$

$$t = \frac{1}{314} \cos^{-1} \left( \frac{100}{141.4} \right) = (2.5 \text{ ms}) \quad \left\{ \text{radian mode} \right\}$$

$$\text{Amplitude } V_m = 141.4 \text{ Volt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 100V \quad \left\{ \text{On comparing} \right\}$$

$$V_{avg} = \frac{2}{\pi} V_m = \frac{2}{\pi} \times 141.4 = 90V$$


$$\text{Form factor } K_f = \frac{V_{rms}}{V_{avg}} = \frac{100}{90} = 1.11$$

## RMS and Average Values of different waveform
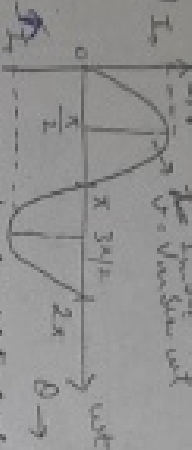
### 1) Sinusoidal Current / Voltage (AKTU 17-18)

Derive an expression for average value & rms value of a sinusoidal varying AC voltage.

$\pm 2\pi$  (length of the base)  
Value say  $\frac{1}{T} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta$



Rms Value  
$$V_{rms} = \frac{1}{2\pi} \int_0^{2\pi} (V^2 \sin^2 \theta) \cdot d\theta$$

$$V_{rms} = \frac{1}{2\pi} \int_0^{2\pi} \frac{2V_m^2 \sin^2 \theta \cdot d\theta}{2}$$

$$= \frac{1}{4\pi} V_m^2 \left[ \int_0^{2\pi} (1 - \cos 2\theta) d\theta \right]$$

$$= \frac{V_m^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}$$

$$V_{rms} = \frac{V_m^2}{4\pi} [2\pi - 0]$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$rms = 0.707 V_m$$

Form factor  $K_F = \frac{V_{rms}}{V_{avg}}$

Peak factor  $K_P = \frac{V_m}{V_{rms}} = \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2} = 1.414$

Average value for complete cycle is zero.

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V \sin \theta d\theta$$

$$= \frac{V_m}{\pi} \int_0^{\pi} \sin \theta d\theta$$

$$= \frac{V_m}{\pi} [-\cos \theta]_0^{\pi}$$

$$= \frac{V_m}{\pi} [-\cos \pi - (-\cos 0)]$$

$$= \frac{V_m}{\pi} [1 + 1]$$

$$V_{avg} = \frac{2V_m}{\pi}$$

OR 
$$V_{avg} = 0.637 V_m$$

$$K_F = \frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{2}}{0.637 V_m} = 1.11$$

## 2) Full wave Rectified Sinusoidal Wave

$\pi \rightarrow$  length of base  
Value say  $\frac{1}{T} = \frac{1}{2\pi} \int_0^{2\pi} V_m |\sin \theta| d\theta$



Rms Value  
$$V_{rms} = \frac{1}{2\pi} \int_0^{2\pi} V^2 \sin^2 \theta \cdot d\theta$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \frac{2V_m^2 \sin^2 \theta \cdot d\theta}{2}$$

$$= \frac{V_m^2}{2\pi} \int_0^{2\pi} \sin^2 \theta d\theta$$

$$= \frac{V_m^2}{2\pi} \int_0^{2\pi} (1 - \cos 2\theta) d\theta$$

$$= \frac{V_m^2}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{2\pi}$$

$$= \frac{V_m^2}{2\pi} [\pi - 0]$$

$$= \frac{V_m^2}{2}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Form factor  $K_F = \frac{V_{rms}}{V_{avg}}$


Peak factor  $K_P = \frac{V_m}{V_{rms}}$

$$K_P = \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2} = 1.414$$

$$V_{avg} = 0.637 V_m$$

### 3- Half wave Rectified Sinusoidal waveform

$2\pi \rightarrow$  length of base

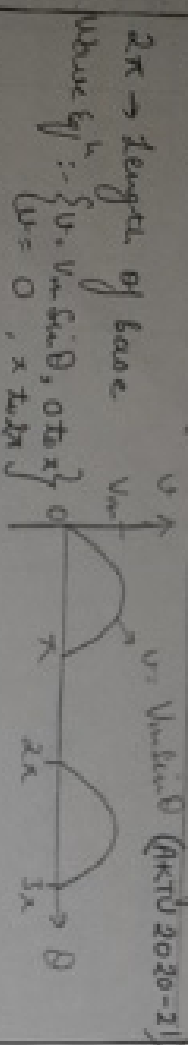

R.M.S Value

$$V_{rms} = \frac{1}{2\pi} \int_0^{2\pi} v^2(\theta) \cdot d\theta$$

$$= \frac{1}{2\pi} \left[ \int_0^{\pi} V_m^2 \sin^2 \theta d\theta + \int_{\pi}^{2\pi} 0 \cdot d\theta \right]$$

$$= \frac{V_m^2}{2\pi} \int_0^{\pi} \frac{2 \sin^2 \theta d\theta}{2}$$

$$= \frac{V_m^2}{4\pi} \left[ \int_0^{\pi} (1 - \cos 2\theta) d\theta \right]$$

$$= \frac{V_m^2}{4\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}$$

$$= \frac{V_m^2}{4\pi} (\pi - 0)$$

$$= \frac{V_m^2}{4}$$


$$\text{or } V_{rms} = \frac{V_m}{2}$$

Form factor  $k_f = \frac{V_{m/2}}{(V_m/\pi)} = 1.57$

Peak factor  $(k_p) = \frac{V_m}{V_{rms}} = \frac{V_m}{V_m/2} = 2$

### 4- SQUARE WAVE FORM :-

Time period  $T = T_{ec}$

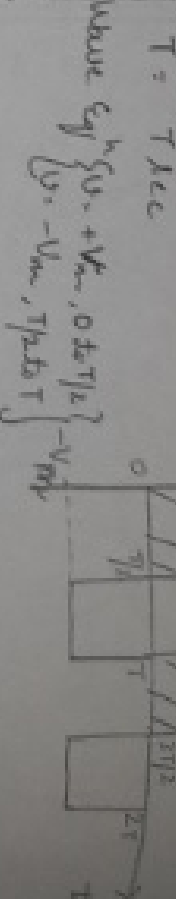

R.M.S Value

$$V_{rms} = \frac{1}{T} \int_0^T v(t) \cdot dt$$

$$= \frac{1}{T} \left[ \int_0^{T/2} V_m dt + \int_{T/2}^T (-V_m) dt \right]$$

$$= \frac{V_m^2}{T} \left[ \int_0^{T/2} 1 \cdot dt + \int_{T/2}^T 1 \cdot dt \right]$$

$$= \frac{V_m^2}{T} \left[ (t)_0^{T/2} + (t)_{T/2}^T \right]$$

$$= \frac{V_m^2}{T} (T)$$

$$= \frac{V_m^2}{T} (T)$$

$$\text{or } V_{rms} = V_m$$

Form factor  $(k_f) = \frac{V_{rms}}{V_m} = \frac{V_m}{V_m} = 1$

Peak factor  $(k_p) = \frac{V_m}{V_{rms}} = \frac{V_m}{V_m} = 1$

Average value

For a complete cycle

$$V_{avg} = \frac{1}{T} \int_0^T v_m dt$$

$$V_{avg} = \frac{1}{T} \cdot V_m \left[ t \right]_0^T$$


$$V_{avg} = \frac{1}{T} \cdot V_m [T - 0]$$

$$V_{avg} = V_m$$

Given find Rms Value, Average Value, Form factor  
Peak factor of the given waveform - (RKTU 2013-14)

Time Period  $T = 0.3 \text{ sec}$
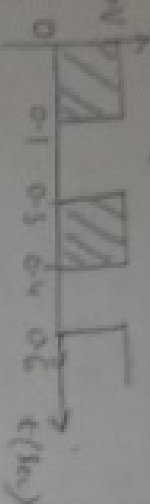
$$\begin{cases} v = 30 \text{ V}, & 0 \leq t < 0.1 \\ v = 0, & 0.1 < t < 0.3 \end{cases}$$



$$V_{rms} = \frac{1}{T} \int_0^T v^2(t) dt$$

$$= \frac{1}{0.3} \left[ \int_0^{0.1} (30)^2 dt + \int_{0.1}^{0.3} 0 dt \right]$$

$$= \frac{1}{0.3} \times 900 [t]_0^{0.1} = \frac{900}{0.3} (0.1)$$

$$= \frac{900}{0.3} (0.1) = 300 \text{ Volt}$$

$$V_{rms} = \sqrt{300} = 17.32 \text{ Volt}$$

$$\text{Form factor } K_f = \frac{V_{rms}}{V_{avg}} = \frac{17.32}{10} = 1.732$$

$$\text{Peak factor } K_p = \frac{V_m}{V_{rms}} = \frac{30}{17.32} = 1.732$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{0.3} \left[ \int_0^{0.1} 30 dt + \int_{0.1}^{0.3} 0 dt \right]$$

$$= \frac{30}{0.3} (t) \Big|_0^{0.1} = \frac{30}{0.3} (0.1) = 10 \text{ Volt}$$

$$V_{avg} = 10 \text{ Volt}$$

$$V_{rms} = 17.32 \text{ Volt}$$

$$K_f = \frac{V_{rms}}{V_{avg}} = \frac{17.32}{10} = 1.732$$

$$K_p = \frac{V_m}{V_{rms}} = \frac{30}{17.32} = 1.732$$


5) Sawtooth Waveform

$T$  Time

Equation of wave in  
equation of line (OA)

$$y = m x, y = \left( \frac{y_2 - y_1}{x_2 - x_1} \right) \cdot x$$
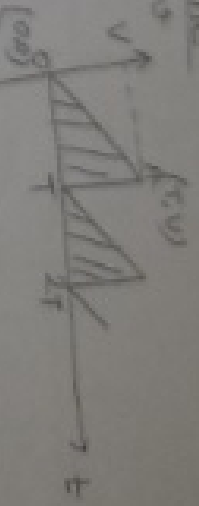
$$v = \frac{V}{T} \cdot t \quad \text{--- (1)}$$



RMS Value

$$V_{rms} = \frac{1}{T} \int_0^T v^2(t) \cdot dt$$

$$= \frac{1}{T} \int_0^T \left( \frac{V}{T} \cdot t \right)^2 \cdot dt$$

$$= \frac{V^2}{T^3} \cdot \left[ \frac{t^3}{3} \right]_0^T$$

$$\text{or } V_{rms} = \frac{V_m}{\sqrt{3}}$$

$$\text{Average Value}$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) \cdot dt$$

$$= \frac{1}{T} \int_0^T \frac{V}{T} \cdot t \cdot dt$$

$$= \frac{V}{T^2} \left[ \frac{t^2}{2} \right]_0^T$$


$$\text{or } V_{avg} = \frac{V}{2} \text{ or } \frac{V_m}{2}$$

$$K_f = \frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{3}}{V_m/2} = 1.15$$

$$K_p = \frac{V_m}{V_{rms}} = \frac{V_m}{V_m/\sqrt{3}} = \sqrt{3} = 1.73$$

Prob 1: Find  $V_{rms}$ ,  $V_{avg}$ ,  $K_F$ ,  $K_P$  for the given wave

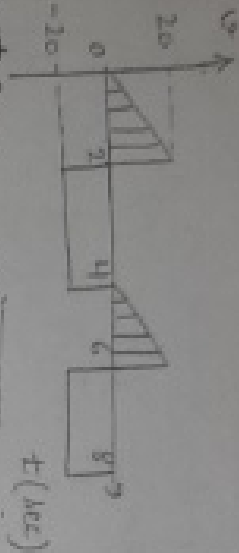sol<sup>n</sup>  
Time Period (T) = 4 sec



$$v = 10t \text{ for } t = 0 \text{ to } 2 \text{ sec}$$

$$v = -20 \text{ for } t = 2 \text{ to } 4 \text{ sec}$$

$$V_{rms} = \frac{1}{T} \int_0^T v^2(t) \cdot dt = \frac{1}{4} \left[ \int_0^2 (10t)^2 dt + \int_2^4 (-20)^2 dt \right]$$

$$= \frac{1}{4} \left[ \frac{100}{3} t^3 \Big|_0^2 + 400 [t]_2^4 \right]$$

$$= \frac{1}{4} \left[ \frac{100 \times 8}{3} + 400 [4 - 2] \right]$$

$$V_{rms} = \frac{1}{4} \left[ \left( \frac{100 \times 8}{3} \right) + (400 \times 2) \right]$$

$$V_{rms} = \sqrt{266.66} = 16.32 \text{ Volt}$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{4} \left[ \int_0^2 10t dt + \int_2^4 (-20) dt \right]$$

$$= \frac{1}{4} \left[ 10 \times \left[ \frac{t^2}{2} \right]_0^2 + (-20) (t) \Big|_2^4 \right]$$

$$= \frac{1}{4} \left[ (10 \times \frac{4}{2}) - 20 \times 2 \right]$$


$$= \frac{1}{4} [20 - 40] = -5 \text{ Volt}$$

$$K_F: \frac{V_{rms}}{V_{avg}} = \frac{16.32}{5} = 3.26$$

$$K_P = \frac{V_m}{V_{rms}} = \frac{20}{16.32} = 1.22$$

Prob 2: Find  $I_{rms}$ ,  $I_{avg}$ ,  $K_F$  &  $K_P$ . A.T.W (20/15)
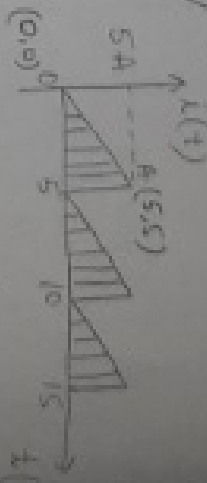
$$I(t) = \frac{I_m}{T} \cdot t = \frac{5}{5} \cdot t = t$$



Eq<sup>n</sup> of wave  
 $i(t) = m \cdot x$

$$i(t) = \frac{5-0}{5-0} \cdot t$$

$$[i(t) = t]$$

$$I_{rms} = \frac{1}{T} \int_0^T i^2(t) dt$$

$$= \frac{1}{5} \int_0^5 t^2 dt = \frac{1}{5} \left[ \frac{t^3}{3} \right]_0^5$$

$$I_{rms} = \frac{1}{5} \left[ \frac{125}{3} \right]$$

$$I_{rms} = 2.88 \text{ A}$$


Form factor  $K_F$

$$K_F = \frac{I_{rms}}{I_{avg}} = \frac{2.88}{2.5} = 1.152$$

Peak factor  $K_P$

$$K_P = \frac{I_{max}}{I_{rms}} = \frac{5}{2.88} = 1.73$$

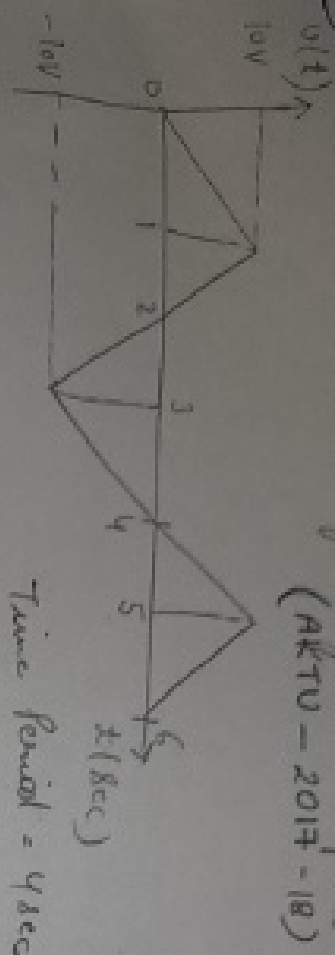Q. 1. Determine Form factor of the given waveform (AKTU - 2017-18)



For a symmetrical waveform, average value over a complete cycle is zero.  
So for half cycle -

Area under the curve for half cycle =  $\frac{1}{2} \times 2 \times 10$

base of half cycle


$$V_{avg} = 5 \text{ volt}$$

$$\frac{1}{T} \int_0^T v^2(t) \cdot dt = \frac{1}{2} \int_0^2 2 \times \int_0^2 v^2(t) \cdot dt \quad \text{--- (1)}$$

line AB, eq<sup>n</sup> of line is  $y = mx$

$$v(t) = \frac{10-0}{1-0} \cdot t$$

$$v(t) = 10t \quad \text{--- (2)}$$

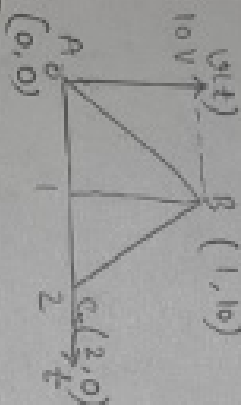

B. Tech I Year [Subject Name: Electrical Engineering]

For line BC,  $v(t) = mx + c$   
 $v(t) = \frac{(10-0)}{(1-2)} \cdot t + c$

$$v(t) = -10t + c \quad \text{--- (3)}$$

For point (2,0)  
 $0 = -10 \times 2 + c$   
 $(c = 20)$

Hence line BC,  $v(t) = -10t + 20$  --- (4)

$$\text{From eq (1)} \left\{ \int_0^2 v^2(t) \cdot dt \right\} = \int_0^1 (10t)^2 \cdot dt + \int_1^2 (-10t + 20)^2 \cdot dt$$

$$= \int_0^1 100t^2 \cdot dt + \int_1^2 (100t^2 - 400t + 400) \cdot dt$$

$$= \left[ \frac{100}{3} t^3 \right]_0^1 + \left[ \frac{100}{3} t^3 - 200t^2 + 400t \right]_1^2$$

$$= \frac{100}{3} + \frac{100}{3} (2^3 - 1^3) - 200(2^2 - 1^2) + 400(2 - 1)$$

$$= 66.67$$


So,  $V_{rms} = \frac{1}{2} \sqrt{2 \times 66.67}$

or  $V_{rms} = 5.77 \text{ Volt}$

Form factor  $K_f = \frac{V_{rms}}{V_{avg}} = \frac{5.77}{5} = 1.154$

Ques Find rms value, average value, form factor & peak factor for the given wave

Ans: Time Period = 2 sec

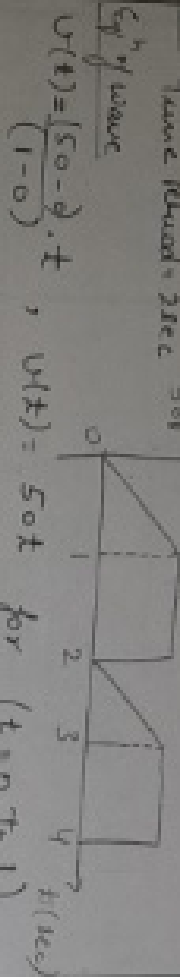

$v(t) = 50$  for  $(t = 1 \text{ to } 2 \text{ sec})$

$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$

$$V_{rms} = \frac{1}{2} \left[ \int_0^1 (50t)^2 dt + \int_1^2 (50)^2 dt \right]$$

$$= \frac{1}{2} \left[ (50)^2 \left[ \frac{t^3}{3} \right]_0^1 + 2500 \left[ t \right]_1^2 \right]$$

$$= \frac{1}{2} \left[ \frac{2500}{3} + 2500 \right] = \frac{10000}{3}$$

or  $V_{rms} = 40.8 \text{ Volt}$

$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{2} \left[ \int_0^1 50t dt + \int_1^2 50 dt \right]$

$$= \frac{1}{2} \left[ 50 \left[ \frac{t^2}{2} \right]_0^1 + 50 \left[ t \right]_1^2 \right]$$

$$= \frac{1}{2} [25 + 50] = \frac{75}{2}$$

or  $V_{avg} = 37.5 \text{ Volt}$

$K_f = \frac{V_{rms}}{V_{avg}} = \frac{40.8}{37.5} = 1.088$

$K_p = \frac{V_{max}}{V_{avg}} = \frac{50}{37.5} = 1.225$

Ques Find form factor of the given waveform

Ans:  $2\pi \rightarrow$  length of the base

Eqn of wave -

$v(\theta) = 100$  , For  $\theta = 0 \text{ to } \theta = \pi$   
 $v(\theta) = 100 \sin \theta$  , For  $\theta = \pi \text{ to } \theta = 2\pi$

For Function take +ve sign.

$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 \theta d\theta}$

$$V_{rms} = \frac{1}{2\pi} \left[ \int_0^\pi (100)^2 d\theta + \int_\pi^{2\pi} (100 \sin \theta)^2 d\theta \right]$$

$$= \frac{1}{2\pi} \left[ 100^2 \int_0^\pi 1 d\theta + \frac{100^2}{2} \int_\pi^{2\pi} (1 - \cos 2\theta) d\theta \right]$$

$$= \frac{100^2}{2\pi} \left[ \theta \right]_0^\pi + \frac{1}{2} \left\{ \left[ \theta \right]_\pi^{2\pi} - \left[ \frac{\sin 2\theta}{2} \right]_\pi^{2\pi} \right\}$$

$$= \frac{100^2}{2\pi} \left[ \pi + \frac{1}{2} [\pi - 0] \right]$$


$V_{rms} = 50\sqrt{3} = 86.60 \text{ Volt}$

$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} v(\theta) d\theta$

$$= \frac{1}{2\pi} \left[ \int_0^\pi 100 d\theta + \int_\pi^{2\pi} 100 \sin \theta d\theta \right]$$

$$= \frac{100}{2\pi} \left[ \int_0^\pi 1 d\theta + \int_\pi^{2\pi} \sin \theta d\theta \right]$$

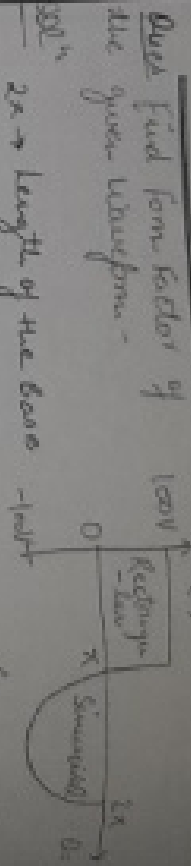$V_{avg} = \frac{18.16 \text{ Volt}}{86.60} = 4.7$



(Unsynchronized)

R.M.S Value of Combined waveform - 2 rms

$i = 10A$  d.c

$i(t) = 12 \sin \omega t + 6 \sin(3\omega t - \frac{\pi}{6}) + 4 \sin(5\omega t + \frac{\pi}{3})$  a.c


R.M.S value of combined a.c & d.c is -

$I_{rms} = (10)^2 + (\frac{12}{\sqrt{2}})^2 + (\frac{6}{\sqrt{2}})^2 + (\frac{4}{\sqrt{2}})^2 = 198$

or  $I_{rms} = 14.07 A_{avg}$

Find form factor of the waveform given - AMTU(14-15)

$v(\theta) = 100 \sin \theta$

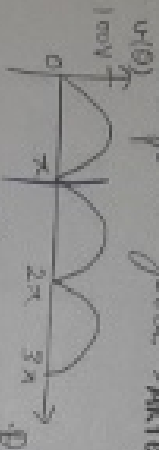

$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^\pi v^2(\theta) \cdot d\theta}$

$V_{rms} = \frac{1}{\pi} \int_0^\pi (100 \sin \theta)^2 d\theta$

$= \frac{100^2}{2\pi} \int_0^\pi 2 \sin^2 \theta d\theta$

$= \frac{100^2}{2\pi} \int_0^\pi (1 - \cos 2\theta) d\theta$

$= \frac{100^2}{2\pi} \left[ \theta - \frac{\sin 2\theta}{2} \right]_0^\pi$

$= \frac{100^2}{2\pi} [\pi - 0]$

$V_{rms} = \frac{100}{\sqrt{2}}$

$V_{avg} = \frac{1}{\pi} \int_0^\pi v(\theta) \cdot d\theta$

$= \frac{100}{\pi} \left[ (-\cos \theta) \right]_0^\pi$

$= \frac{100}{\pi} [-\cos \pi + \cos 0]$

$= \frac{100}{\pi} [ -(-1) + 1 ]$

$V_{avg} = \frac{200}{\pi}$

$K_F = \frac{V_{rms}}{V_{avg}} = \frac{100/\sqrt{2}}{200/\pi} = 1.11$

$K_p = \frac{V_m}{V_{rms}} = \frac{100}{100/\sqrt{2}} = \sqrt{2} = 1.414$

Concept of Phase and Phase difference


a.c  $\rightarrow A \sin \omega t$  (Phase) Polar Form:  $A \angle \phi \rightarrow$  Phase

Magnitude

$A \angle \phi$

Rectangular =  $A + jB$   
Real Imaginary


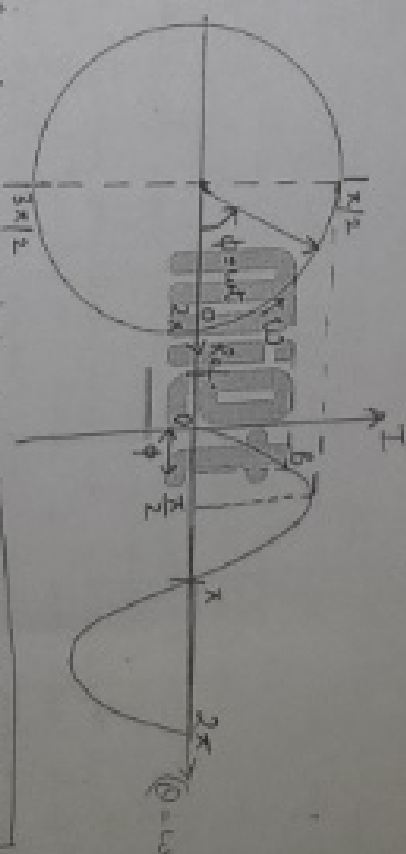
Phase: Phase of an alternating quantity at any instant is the angle ( $\phi$ ) travelled by the phasor representing that alternating quantity upto the instant of consideration, measured from the reference.




Equation of ac is given by  $e = E_m \sin(\omega t \pm \phi)$

Three cases are -

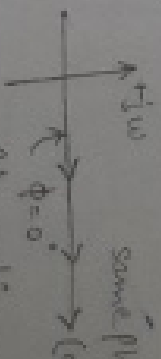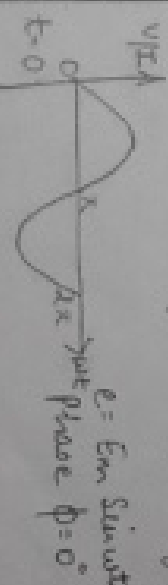Case I ( $\phi = 0^\circ$ )  $\rightarrow$  Zero phase means at  $t=0$ , instantaneous value of ac quantity is zero.



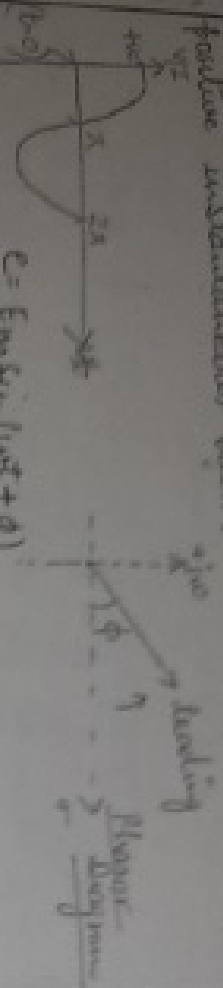Case 2 Positive Phase :- If at  $t = 0$ , alternating quantity has positive instantaneous value.




Case 3 Negative Phase :- If at  $t = 0$ , alternating quantity has negative instantaneous value.



Phase is measured w.r.t reference direction i.e. +ve x-axis direction.


Phase measured in anticlockwise direction is +ve while measured in clockwise direction is negative. The difference b/w the phases of the two alternating quantities is called the Phase Difference.

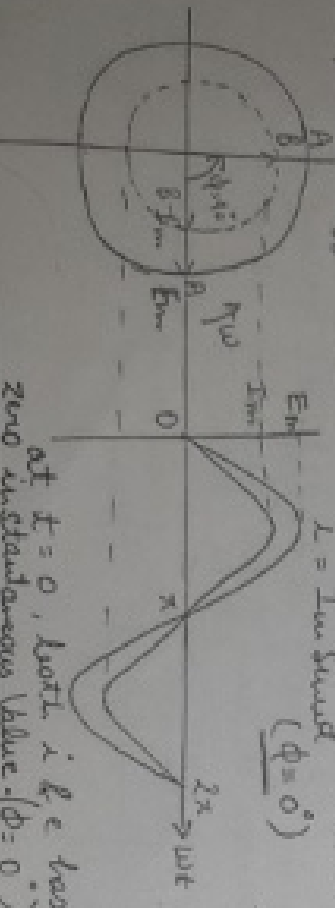1) Zero Phase Difference :-  $e = E_m \sin \omega t$   
 $i = I_m \sin \omega t$  ( $\phi = 0^\circ$ )




at  $t = 0$ , both  $e$  &  $i$  are zero instantaneous value ( $\phi = 0^\circ$ )

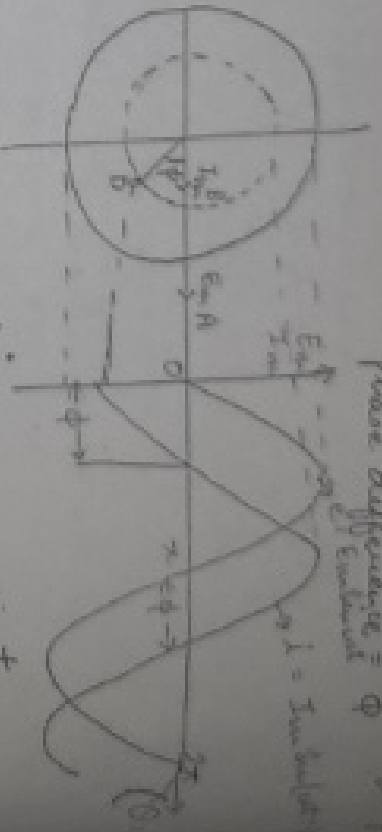
Lagging Phase Difference :-  $e = E_m \sin \omega t$   
 $i = I_m \sin(\omega t - \phi)$   
 $e$  leads  $i$  by ' $\phi$ ', or  $i$  lags  $e$  by ' $\phi$ '.  
Phase difference =  $\phi$



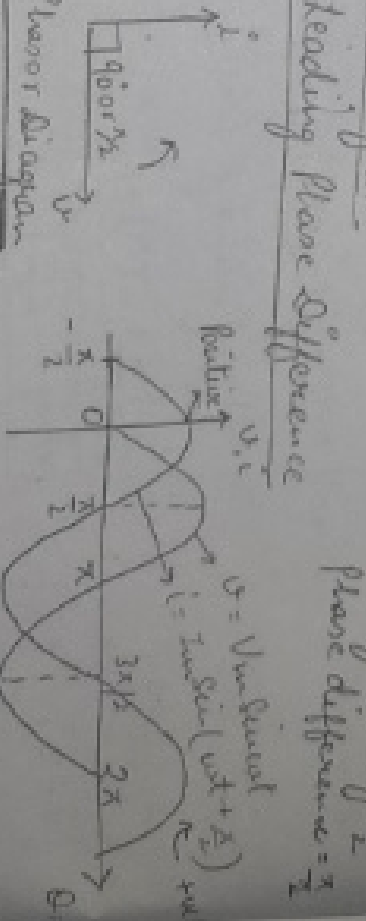Leading Phase Difference  
 $e = E_m \sin \omega t$   
 $i = I_m \sin(\omega t + \phi)$   
 $i$  leads  $e$  by ' $\phi$ '  
Phase difference =  $\phi$



Same Phase :- ( $\phi = 0^\circ$ )

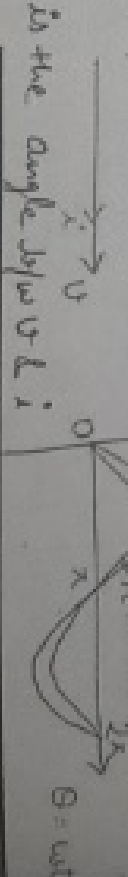

$\phi$  is the angle b/w  $v$  &  $i$

Draw the Phasor Diagram of the following voltages & find their value of resultant voltage

$V_1 = 100 \sin \omega t$  rms value of resultant voltage

$V_2 = 200 \sin(\omega t + \frac{\pi}{3})$  Polar Form  $200 \angle 60^\circ$

$V_3 = 50 \cos \omega t$   $50 \cos \omega t = 50 \sin(\omega t + \frac{\pi}{2})$   $50 \angle 90^\circ$

$V_4 = 50 \sin(\omega t - \frac{\pi}{4})$   $50 \sin(\omega t - \frac{\pi}{4}) = 50 \angle -45^\circ$

Resultant Voltage  $\vec{V} = \vec{V}_1 + \vec{V}_2 + \vec{V}_3 + \vec{V}_4$

$\vec{V} = [70.71 \angle 0^\circ + 141.42 \angle 60^\circ + 35.35 \angle 90^\circ + 106.06 \angle -45^\circ]$

Convert to Rectangular form

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

$\vec{V} = [70.71 + j0] + [70.71 + j60.62] + [0 - j35.35] + [75.52 - j75.52]$

Multiplication and Division of Phasors -

Given for the two phasors  $A = a_1 + jb_1$ , and  $B = a_2 + jb_2$  obtain their multiplication & division using polar form

$A = a_1 + jb_1$   $B = a_2 + jb_2$

For Multiplication & division, use polar co-ordinates

$A = |A| \angle \phi_1 = \sqrt{a_1^2 + b_1^2} \angle \tan^{-1} \frac{b_1}{a_1}$

$B = |B| \angle \phi_2 = \sqrt{a_2^2 + b_2^2} \angle \tan^{-1} \frac{b_2}{a_2}$

$A \times B = |A| |B| \angle \phi_1 \angle \phi_2$

$\frac{A}{B} = \frac{|A| \angle \phi_1}{|B| \angle \phi_2} = \frac{|A|}{|B|} \angle \phi_1 - \phi_2$

Given three currents  $I_1 = 20 \sin(\omega t - \frac{\pi}{6})$ ,  $I_2 = 30 \sin(\omega t + \frac{\pi}{4})$ , Find Magnitude & Phase angle of resultant current of their addition.

$I_1 = 20 \sin(\omega t - \frac{\pi}{6})$  i.e.  $I_1 = 20 \angle -30^\circ$

$I_2 = 30 \sin(\omega t + \frac{\pi}{4})$  i.e.  $I_2 = 30 \angle 45^\circ$

$I_3 = 10 \sin \omega t$  i.e.  $I_3 = 10 \angle 0^\circ$

$I_1 = (10 + j0) A$ ,  $I_2 = (17.32 - j10) A$ ,  $I_3 = (10 + j0) A$

$I_R = I_1 + I_2 + I_3$

$I_R = 10 + j0 + 17.32 - j10 + 10 + j0$

$I_R = 37.32 \angle 13^\circ$

Magnitude = 37.32 A, Phase Angle =  $13^\circ$

## PURELY RESISTIVE CIRCUIT (R Only) :-

Let 'Z' be the impedance of the circuit.

Current flowing through the circuit -  

$$i = \frac{V}{Z} = \frac{V_m \sin \omega t}{Z}$$

$Z = \text{Im. circuit}$

Or  $I_{rms} = \frac{V_m}{Z} = \frac{V_m}{R}$

$Z = R$   $\Omega$

- 1) Impedance  $Z = R$   $\Omega$
- 2)  $\phi = 0^\circ$  (Same phase)
- 3) Power factor  $(\cos \phi = \cos 0 = 1)$  i.e. unity
- 4)  $V$  &  $i$  are in same phase

$\phi = 0^\circ$  (Same phase)

## POWER :-

$P = V \cdot i$

$P = V_m \sin \omega t \cdot I_m \sin \omega t$

$P = \frac{V_m I_m \sin^2 \omega t}{2}$

$P = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$


$P = \frac{V_m I_m \cos 2\omega t}{2}$

$P = \frac{V_m I_m}{2} \cos 2\omega t$

$P = \frac{V_m I_m}{2} \cos 2\omega t$

$P = \frac{V_m I_m}{2} \cos 2\omega t$

$P = \frac{V_m I_m}{2} \cos 2\omega t$

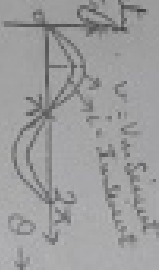

Average Power over a complete cycle in

$P_{avg} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$


$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

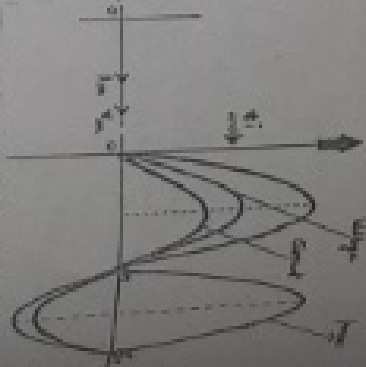$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$



$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$P_{avg} = \frac{V_{rms} \cdot I_{rms}}{2}$

$$i_{rms} = \frac{V_m}{Z} = \frac{V_m}{X_L}$$

$$Z = X_L = \omega L = 2\pi fL \quad (\Omega)$$

$$1) \text{ Impedance } (Z = X_L) \rightarrow$$

$$2) \text{ Phase } \phi \text{ lag } \frac{\pi}{2} \text{ or } 90^\circ \text{ (i.e. } \phi = 90^\circ)$$

$$3) \text{ Power factor } \cos \phi = \cos \frac{\pi}{2} = 0$$

$$4) \text{ Power } (P) = VI \cos \phi$$

$$P = 0 \quad [\because \cos \phi = 0]$$

$$V = V_m \sin \omega t = V \sin \omega t$$

$$i = I_m \sin(\omega t - 90^\circ) = I \sin \omega t$$

$$\text{Impedance } Z = \frac{V}{I}$$

$$Z = X_L \angle 90^\circ \text{ or } (0 + jX_L) = j\omega L$$

Let P.F. is lagging.

Inductive reactance is

offered as the opposition offered by inductance of a circuit to the flow of alternating sinusoidal current.

### \* POWER :-

$$P = V \cdot I$$



$$P = V_m I_m \sin \omega t \cdot I_m \sin(\omega t - \frac{\pi}{2})$$

$$P = -\frac{V_m I_m}{2} 2 (\sin \omega t \cdot \cos \omega t)$$

$$P = -\frac{V_m I_m}{2} \sin 2 \omega t$$

$$P_{avg} = \left[ \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \sin 2 \omega t dt \right]$$

$$P_{avg} = 0$$

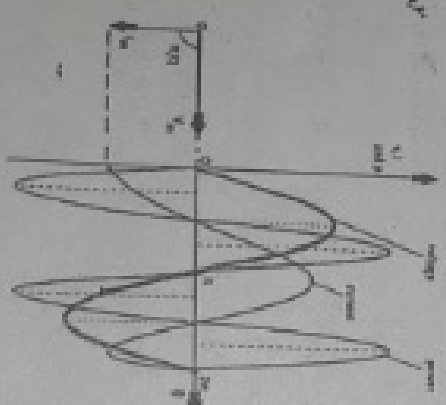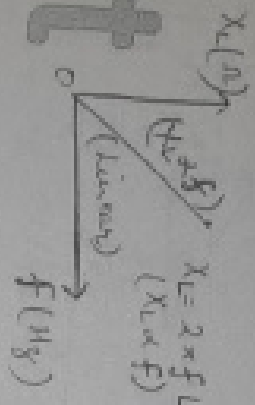

### B. Tech I Year [Subject Name: Electrical Engineering]

### PURELY CAPACITIVE CIRCUIT (C Only) 215-163

Let a pure capacitor (C) is connected to an a.c. sinusoidal voltage  $V_m \sin \omega t$  the instantaneous charge 'q' on plates of the capacitor is

$$q = C V$$

$$\text{Current } i = \frac{dq}{dt} = \frac{d}{dt} (C V)$$

$$i = C \frac{dV}{dt} = C \frac{d}{dt} (V_m \sin \omega t)$$

$$i = C \omega V_m \cos \omega t$$

$$i = \frac{V_m}{X_C} \sin(\omega t + \frac{\pi}{2})$$

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$

$$i \text{ leads } V \text{ by } \frac{\pi}{2} \text{ or } 90^\circ$$

$$i = \frac{V_m}{Z} = \frac{V_m}{\omega C} = \frac{V_m}{X_C}$$

$$Z = X_C = \frac{1}{\omega C} \quad (\Omega)$$

$$\phi = 90^\circ, i \text{ leads } V \text{ by } 90^\circ$$

$$\cos \phi = \cos 90^\circ = 0$$

$$\text{Power } (P) = 0 \text{ as } \cos \phi = 0$$

$$\text{IMEDANCE :- } (Z)$$

$$V = V_m \sin \omega t = V \sin \omega t$$

$$i = I_m \sin(\omega t + \frac{\pi}{2}) = I \sin \omega t$$

$$Z = \frac{V}{I} \angle 90^\circ = (0 - jX_C) \Omega$$

$$Z = \frac{V}{I} \angle 90^\circ = X_C \angle -90^\circ = (0 - jX_C) \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$


$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

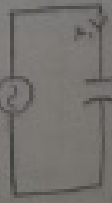

$$V = V_m \sin \omega t$$

### POWER

$$P = V \cdot I$$

$$P = V_m I_m \sin \omega t \cdot I_m \sin(\omega t + \frac{\pi}{2})$$

$$P = \frac{V_m I_m}{2} 2 (\sin \omega t \cdot \cos \omega t)$$

$$P = \frac{V_m I_m}{2} \sin 2 \omega t$$

$$P_{avg} = \left[ \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \sin 2 \omega t dt \right]$$

$$P_{avg} = 0$$

$$P_{avg} = 0 \rightarrow \text{Average power in a purely capacitive circuit is zero.}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$


$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$


$$X_C \propto \frac{1}{f}$$

$$X_C \propto \frac{1}{f}$$

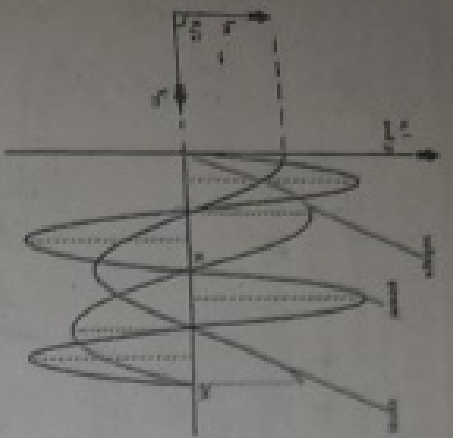
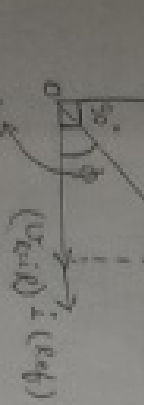
### Series R-L Circuit (Inductive ckt)

$\vec{V} = \vec{V}_R + \vec{V}_L$  — (1)  
 $V_R$  is in phase with  $i$  for  $R$   
 $V_L$  leads  $i$  by  $90^\circ$  for  $L$



( $0 < \phi < 90^\circ$ )  
 From phasor diagram -  
 'i' lags 'V' by  $\phi$ .  
 $V = I_m \sin \omega t$   
 $i = I_m \sin(\omega t - \phi)$

From the fig. below -  
 $V^2 = V_R^2 + V_L^2$   
 $(iZ)^2 = (iR)^2 + (iX_L)^2$

$|Z| = \sqrt{R^2 + X_L^2}$   
 Impedance  $Z$

$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR}$   
 $\therefore \phi = \tan^{-1} \frac{X_L}{R}$

\*  $\cos \phi$  (Power Factor) =  $\frac{V_R}{V} = \frac{IR}{iZ}$   
 $\cos \phi = \frac{R}{Z}$

$R = Z \cos \phi$   
 $\sin \phi = \frac{V_L}{V} = \frac{IX_L}{iZ}$   
 $X_L = \frac{Z \sin \phi}{\sin \phi}$

or  $X_L = Z \sin \phi$

### Impedance (Z) :-

$V = VI \cos \phi$   
 $I = I \cos \phi$

$Z = \frac{V}{I} = \frac{V}{I \cos \phi}$

$|Z| = \frac{\sqrt{R^2 + X_L^2}}{\cos \phi}$   
 Conf. is lagging ( $0 < \phi < 90^\circ$ )  
 R-L ckt

$Z = (R + jX_L) \Omega$



### POWER :-

$P = V \cdot I \cdot \cos \phi$   
 $P = V_m I_m \sin \omega t \cdot I_m \sin(\omega t - \phi)$

$P = \frac{V_m I_m}{2} \{ 2 \sin \omega t \cdot \sin(\omega t - \phi) \}$

$P = \frac{V_m I_m}{2} \{ \cos \phi - \cos(2\omega t - \phi) \}$

$P = \frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos(2\omega t - \phi)$

Constant Part

Avg Power Over a complete cycle

$P_{avg} = \frac{1}{T} \int_0^T \left\{ \frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos(2\omega t - \phi) \right\} dt$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

$P_{avg} = \frac{V_m I_m}{2} \cos \phi$

B. C. Series Circuit (Capacitive Ckt)

$$V^2 = V_R^2 + V_C^2$$

$V_C = iR$  Volt Supply Impedance

$V_C = iX_C$  Volt Supply Impedance

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$


$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

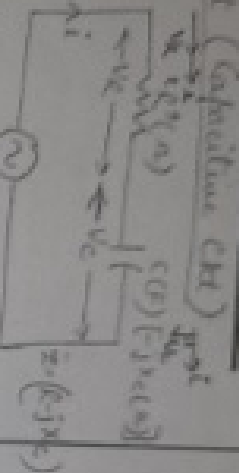$V_C \rightarrow$  lags by  $90^\circ$  for  $C$



From Phasor diagram -

$$V^2 = V_R^2 + V_C^2$$

$$(iZ)^2 = (iR)^2 + (iX_C)^2$$

$$|Z| = \sqrt{R^2 + X_C^2} \quad (\Omega)$$

Phase angle  $\phi$  is given by

$$\tan \phi = \frac{-V_C}{V_R} = \frac{-iX_C}{iR}$$

$$\phi = -\tan^{-1} \left( \frac{X_C}{R} \right)$$

Power factor

$$P.F. = \cos \phi = \frac{R}{Z}$$

Real Power

$$P = V \cdot I \cdot \cos \phi$$

Reactive Power

$$Q = V \cdot I \cdot \sin \phi$$

Complex Power

$$S = V \cdot I$$

Impedance Triangle

B. C. Series Circuit (Inductive Ckt)

$V_C = iR$  Volt Supply Impedance

$V_C = iX_C$  Volt Supply Impedance

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$


$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

$V_C \rightarrow$  lags by  $90^\circ$  for  $C$

$V_C \rightarrow$  is in phase with  $i$  for  $R$

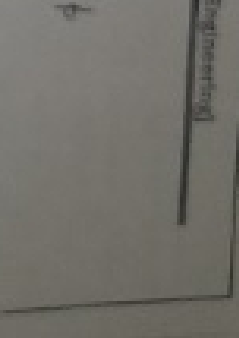$V_C \rightarrow$  lags by  $90^\circ$  for  $C$



From Phasor diagram -

$$V^2 = V_R^2 + V_L^2$$

$$(iZ)^2 = (iR)^2 + (iX_L)^2$$

$$|Z| = \sqrt{R^2 + X_L^2} \quad (\Omega)$$

Phase angle  $\phi$  is given by

$$\tan \phi = \frac{V_L}{V_R} = \frac{iX_L}{iR}$$

$$\phi = \tan^{-1} \left( \frac{X_L}{R} \right)$$

Power factor

$$P.F. = \cos \phi = \frac{R}{Z}$$

Real Power

$$P = V \cdot I \cdot \cos \phi$$

Reactive Power


$$Q = V \cdot I \cdot \sin \phi$$

Complex Power

$$S = V \cdot I$$

Impedance Triangle

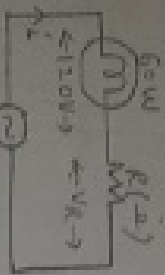Ques: A 120 V, 60 W lamp is to be operated on 230V, 50Hz supply mains. In order that lamp should operate on correct voltage, calculate the value of (a) Max. Inductance (b) Pure Inductance.



Lamp is purely  $R$ .  
 $i = \frac{P}{V_{\text{lamp}}} = \frac{60}{120} = 0.5 \text{ Amp}$

$V_{\text{supply}} = V_{\text{lamp}} + V_L$  (Same Phase)  
 $220 = 120 + V_L$


$V_L = 100 \text{ V}$

$V_L = iR$

$100 = 0.5 R$

$R = 200 \Omega$

(AKTU 2013-14)

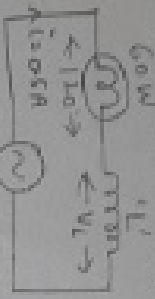

$V_{\text{supply}} = V_{\text{lamp}} + V_L$   
 $V = V_{\text{lamp}} + V_L$

$V_L = \sqrt{(220)^2 - (120)^2}$

$V_L = 184.3908 \text{ Volt}$

$V_L = iX_L$

$184.39 = 0.5 X_L$

$X_L = 368.78 \Omega$

$L = \frac{X_L}{2\pi f} = \frac{368.78}{314}$


$L = 1.1738 \text{ H}$

Ques: A metal filament lamp rated at 750W, 100V is to be connected in series with a capacitance across a 230V, 50Hz supply. Cal. the value of capacitance required. Draw phasor diagram.

$P = VI$

$I = \frac{P}{V} = \frac{750}{100} = 7.5 \text{ amp}$

$I = 7.5 \text{ Amp}$

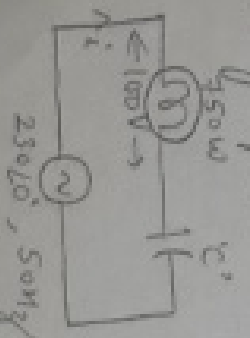

From Phasor Diagram:-

$V^2 = V_{\text{lamp}}^2 + V_C^2$

$(230)^2 = (100)^2 + V_C^2$

$V_C = \sqrt{(230)^2 - (100)^2}$

$V_C = 207.12 \text{ Volt}$

$V_C = iX_C$

$X_C = \frac{V_C}{i} = \frac{207.12}{7.5} = 27.616 \Omega$

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

$C = \frac{1}{115 \cdot 2\pi \cdot 50} = 1.15 \mu\text{F}$

V. Imp: Series R-L-C Circuit (AKTU 2013-14)

According to Kirchhoff's law:

$V = V_R + V_L + V_C$  (1)

$V_R = iR \text{ Volt}$

$V_L = iX_L \text{ Volt}$

$V_C = iX_C \text{ Volt}$

$V_R$  is in phase with  $i$ .

$V_L$  leads  $i$  by  $90^\circ$

$V_C$  lags  $i$  by  $90^\circ$



From Phasor Diagram:-

$V^2 = V_R^2 + (V_L - V_C)^2$


$\{Z = R + j(X_L - X_C)\} \Omega$

$Z = \frac{V}{i} = \frac{V_R + j(V_L - V_C)}{i}$

$Z = \frac{R + j(X_L - X_C)}{1}$

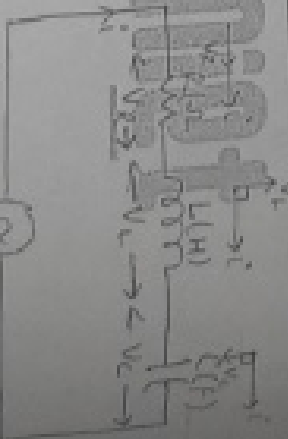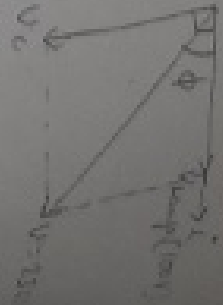

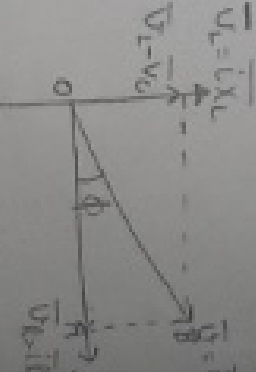$V = V_m \sin \omega t$   
 $V = V \sin \omega t$



Phasor Diagram



### Active (Real) Power (P) :-

It is the power utilized by the ckt. It is the power dissipated in pure resistance.


It is the multiplication of voltage & real component of current.

Flows from source to load.

$P = V_{rms} I_{rms} \cos \phi$  watt

Reactive Power (Q) :- Power which is not utilized by the ckt is called reactive power. It is the multiplication of voltage & reactive component of current.

$Q = V_{rms} I_{rms} \sin \phi$  var

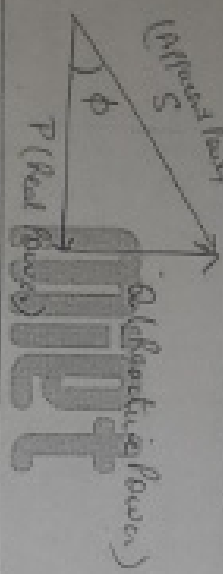

Given  $V = 200 \sin 377t + 10^\circ$  V,  $i = 8 \sin (377t - 30^\circ)$  A.

for pure ckt. Determine :- (a) Impedance (b) ckt elements (c) Power factor (d) P, Q, S (e) Phasor Diagram.

$V_{rms} = 200/\sqrt{2} = 141.42$  V  
 $I_{rms} = 8/\sqrt{2} = 5.66$  A

$\phi = 37^\circ$  lead / sec

$Z = \frac{V}{I} = \frac{200 \angle 10^\circ}{5.66 \angle -30^\circ} = 35.34 \angle 40^\circ \Omega$

$Z = (21.65 + j12.5) \Omega$


$R = 21.65 \Omega$

$X_L = 12.5 \Omega$

$X_L = \omega L$

Imp: A non-inductive resistance of 10  $\Omega$  is connected in series with an inductive coil across 200V, 50Hz supply. The current drawn by the series combination is 10A. The resistance of the coil is 2  $\Omega$ . Determine (a) Inductance of the coil (b) Power factor (c) Voltage across the coil.

(MKTU 2017-18)

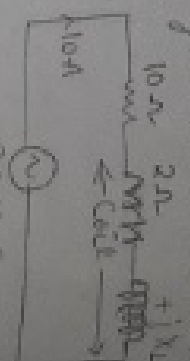

$Z = (R + jX_L) = (12 + jX_L) \Omega$

$121 = \sqrt{12^2 + X_L^2}$   
 $I = 10$   
 $I = \frac{V}{Z}$   
 $10 = \frac{200}{\sqrt{12^2 + X_L^2}}$

$\sqrt{12^2 + X_L^2} = 20$   
 $12^2 + X_L^2 = 400$   
 $X_L^2 = 400 - 144 = 256$   
 $X_L = 16 \Omega$

$X_L = 2\pi fL$   
 $16 = 2\pi \times 50 \times L$   
 $L = 0.06369$  H

$V_{coil} = I \cdot Z_{coil}$   
 $Z_{coil} = R + jX_L = (2 + j16) \Omega = 16.12 \angle 83.7^\circ \Omega$

$V_{coil} = 10 \times 16.12 = 161.2$  Volt

$V_{coil} = 10 \times 16.12 = 161.2$  Volt

Find (i)  $Z$  (ii)  $P$  (iii)  $\cos \phi$

(iv)  $V_R, V_L, V_C$  (v)  $P, Q, S$

$X_L = \omega L = 2\pi \times 50 \times \frac{1}{3} = 1 \Omega$

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi \times 50 \times 1} = 1 \Omega$


$Z = R + j(X_L - X_C) = 10 + j(1 - 1) = 10 \Omega$

$Z = (10 - j1) = 10.04 \angle -5.71^\circ$

$I = \frac{V}{Z} = \frac{200 \angle 0^\circ}{10.04 \angle -5.71^\circ} = 19.92 \angle 5.71^\circ$  A

$I = 19.92 \angle 5.71^\circ$  A

## RESONANCE IN SERIES R-L-C CIRCUIT :-

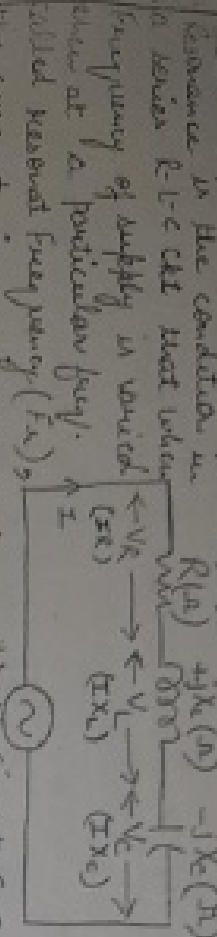

Resonance is the condition in a series R-L-C ckt that when frequency of supply is varied then at a particular freq. called resonant frequency ( $f_r$ ), the current is maximum and net reactance of the ckt is zero. It behaves as a purely resistive ckt and power factor is unity.

At Resonant Frequency  $f_r$ ,

$$V_L - V_C = 0$$

$$X_L = X_C$$

$$I_{X_L} = I_{X_C}$$

$$Z = R$$

$$V = V_C$$

Current is maximum

$$I_{max} = \frac{V}{R}$$

$$\cos \phi = 1$$

$$V' I = 0$$

Voltage & current are in same phase.

Resonant Frequency :- ( $f_r$ )

Frequency at which resonance occurs is called Resonant Frequency ( $f_r$ ).

$$X_L - X_C = 0$$

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$


As  $\omega = 2\pi f$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

Page 38

## RESONANCE CURVE :-

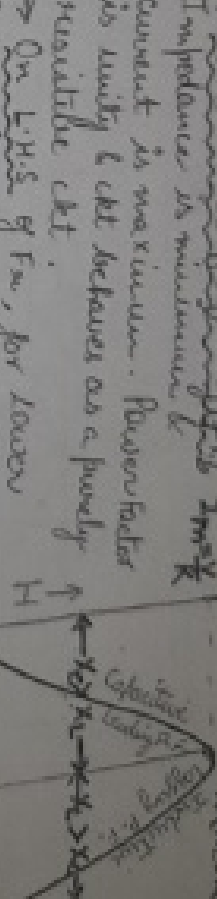

At resonance frequency ( $f_r$ )  $I_{max}$  Impedance is minimum & current is maximum. Power factor is unity & ckt behaves as a purely resistive ckt.

On L.H.S of  $f_r$ , for lower frequencies  $X_C > X_L$  ( $X_C \propto \frac{1}{f}$ ) so ckt behaves as a capacitive ckt & power factor is leading.

On R.H.S of  $f_r$  for higher frequencies  $X_L > X_C$  ( $X_L \propto f$ ) so ckt behaves as an inductive ckt & power factor is lagging.

Ques: Why in series resonance, voltage across L & C is very high?

Ans: In series resonance, current is maximum  $I_{max}$  &  $V_L = V_C$  are very high from supply and voltage.

Ques: Why series R-L-C ckt at resonance is called acceptor ckt?

Ans: In series R-L-C ckt, at resonant frequency, impedance is minimum  $Z = R$  and current is maximum  $I_{max}$ . So, it accepts the signals of a particular frequency. Hence it is called acceptor ckt.

Ques: What are the applications of series resonant circuit?

Ans: In series resonant circuit, it is used in radio transmitters and receivers.

→ In transmitters.

→ Tuning circuits in T.V receivers.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

→ As a wave trap.

Ques:- Devise the Quality factor of series resonant circuit. A-factor is defined as the voltage magnification in a series resonance (voltage resonance) circuit.

A - Voltage across L or C  
Supply Voltage

$$Q = \frac{V}{V}$$

$$Q = \frac{I_{max} \cdot X_L}{I_{max} \cdot R}$$

$$Q = \frac{\omega L}{R}$$

$$Q = \frac{1}{\pi C} \left( \frac{L}{R} \right)$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Ques:- In a series R-L-C circuit,  $R=10\Omega$ ,  $L=0.2H$ ,  $C=40\mu F$ . It is supplied with a 100V supply at variable frequency. Find the following when series resonance circuit:

(i) The frequency at resonance (ii) Current (iii) Power factor

(iv) Power (v) Voltage across R, L, C at resonance.

(vi) Q-factor (vii) Half power frequencies (viii) Phase Diagram.

Given:  $R=10\Omega$ ,  $L=0.2H$ ,  $C=40\mu F$ ,  $V=100V$

Ans: (i)  $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \times 40 \times 10^{-6}}} = 56.269 \text{ (Hz)}$   
(ii)  $I_{max} = \frac{V}{R} = \frac{100}{10} = 10 \text{ (Amp)}$   
(iii)  $\cos\phi = \cos 0^\circ = 1$  (unity) As V & I are in same phase.  
(iv)  $P = I_{max}^2 \cdot R = (10)^2 \times 10 = 1000 \text{ (Watt)}$

(v)  $V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_C = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$V = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_C = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$V = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_C = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$V = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$V = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_C = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$V = I_{max} \cdot X_C = 10 \times 10 = 100 \text{ (V)}$

$V_L = I_{max} \cdot X_L = 10 \times 10 = 100 \text{ (V)}$

$V_R = I_{max} \cdot R = 10 \times 10 = 100 \text{ (V)}$

$$F_1 = 56.269 - 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$


$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

$$F_2 = 56.269 + 3.9788$$

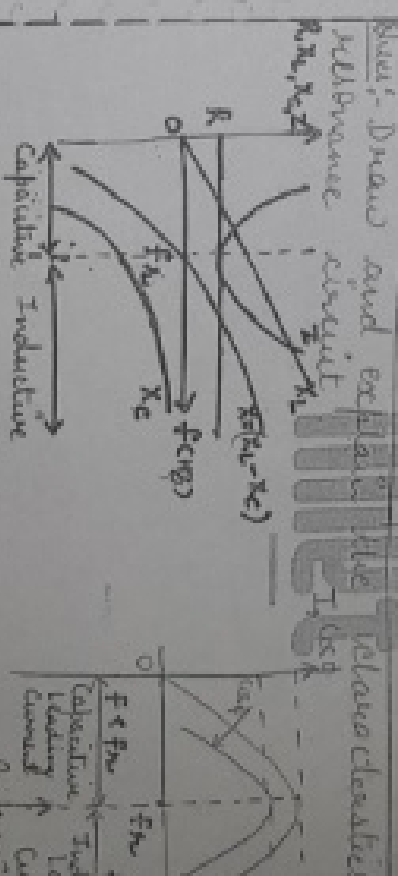

Characteristics of Series Resonance

As  $X_L = 2\pi fL$  i.e.  $X_L \propto f$  & is represented by a straight line from origin.

As  $X_C = \frac{1}{2\pi fC}$  i.e.  $X_C \propto \frac{1}{f}$  & is represented by a hyperbola in fourth quadrant.

$R$  is independent of supply freq. & is represented by a line  $\parallel$  to freq. axis.

$Z$  is independent of supply freq. & is represented by a line  $\parallel$  to freq. axis.

At  $f = f_n$ , value of  $X_L = X_C$  & the net reactance ( $X$ ) curve lies in b/w  $X_L$  &  $X_C$ .

At  $f = f_n$ ,  $\cos\phi = 1$


At  $f < f_n$ ,  $\cos\phi$  is leading in nature

At  $f > f_n$ ,  $\cos\phi$  is lagging in nature.

Before Bandwidth of series R-L-C circuit. Prove that the resonant frequency is the geometric mean of upper & lower half power frequencies.  $f_r = \sqrt{f_1 f_2}$  (Hq).  
 AICTE 2014-18, 16-17, 14-15, 13-14

Bandwidth is defined  $\frac{I_{m/2}}{I_m} \cdot \frac{V}{R}$

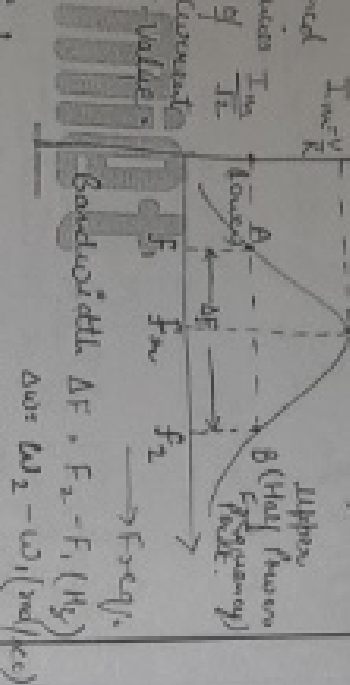As the band of frequencies that lie on either side of resonant freq. where current falls  $\frac{1}{\sqrt{2}}$  times of its max value.



At Half Power Points,  $P_A = P_B = \left(\frac{I_m}{\sqrt{2}}\right)^2 \cdot R$

$$P_A = P_B = \frac{I_m^2 R}{2} = \frac{P}{2}$$

Impedance of R-L-C circuit is given by -

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad (A)$$

$$\text{Current } I = \frac{V}{Z}$$

$$\frac{I_m}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{At Half Power Points } I = \frac{I_m}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I_m = \frac{V}{R} \text{ so } \frac{V}{\sqrt{2} \cdot R} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Squaring both sides -

$$2I^2 = I_m^2 + (X_L - X_C)^2$$

$$R^2 = (X_L - X_C)^2$$

$$R = \pm (X_L - X_C) \quad (B)$$

Case I when  $R = (X_L - X_C)$

$$R = \omega L - \frac{1}{\omega C}$$

$$\omega^2 LC - \omega C R - 1 = 0$$

$$A x^2 + B x + C = 0$$

By Sushdharacharya formula

$$\omega = \frac{-C R \pm \sqrt{C^2 R^2 + 4 L C}}{2 L C}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\omega = \frac{R}{2 L} \pm \sqrt{\frac{R^2}{4 L^2} + \frac{1}{L C}}$$

$$\Delta \omega = \omega_2 - \omega_1 = \frac{R}{L} (\text{rad/sec}) \quad (3)$$

$$\Delta f = f_2 - f_1 = \frac{R}{2\pi L} (\text{cycles/sec}) \quad (4)$$

Put eq (3) in eq (1) & eq (4) in eq (2).

$$\left\{ \begin{aligned} \omega_1 &= \omega_r - \frac{\Delta \omega}{2} \\ \omega_2 &= \omega_r + \frac{\Delta \omega}{2} \end{aligned} \right\} \quad (\text{rad/sec}) \quad (5)$$

$$\left\{ \begin{aligned} f_1 &= f_r - \frac{\Delta f}{2} \\ f_2 &= f_r + \frac{\Delta f}{2} \end{aligned} \right\} \quad (\text{cycles/sec}) \quad (6)$$

To prove that:  $f_r = \sqrt{f_1 f_2}$

We have:

$$\left\{ \begin{aligned} X_L - X_C &= +R \quad (\text{for lower half power}) \\ X_L - X_C &= +R \quad (\text{for upper half power}) \end{aligned} \right\} \quad (7)$$

$$\omega_1 L - \frac{1}{\omega_1 C} = +R \quad (8)$$

$$\omega_2 L - \frac{1}{\omega_2 C} = +R \quad (9)$$

$$X_L - X_C = -R \quad (\text{for lower half power}) \quad (10)$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \quad (11)$$

$$\omega_2 L - \frac{1}{\omega_2 C} = -R \quad (12)$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \quad (13)$$

$$\omega_2 L - \frac{1}{\omega_2 C} = -R \quad (14)$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \quad (15)$$

$$\omega_2 L - \frac{1}{\omega_2 C} = -R \quad (16)$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \quad (17)$$

Ques: In a series R-L-C circuit,  $R = 2\Omega$ ,  $L = 2\text{mH}$ ,  $C = 10\mu\text{F}$ . Find out (i) Resonant frequency (ii) Q-factor (iii) Bandwidth (iv) Half power frequencies (AKTU 2018-19)

Sol: (i)  $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{2 \times 10^{-3} \times 10 \times 10^{-6}}} = 1125.4\text{ Hz}$

(ii) Q-factor  $= \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{2} \sqrt{\frac{2 \times 10^{-3}}{10 \times 10^{-6}}} = 7.07$

(iii) Bandwidth  $\Delta f = \frac{R}{2\pi L} = \frac{2}{2\pi \times 2 \times 10^{-3}} = 159.15\text{ Hz}$

(iv)  $f_1 = f_r - \frac{\Delta f}{2} = 1125.4 - \frac{159.15}{2} = 1043.2\text{ Hz}$

$f_2 = f_r + \frac{\Delta f}{2} = 1125.4 + \frac{159.15}{2} = 1209.6\text{ Hz}$

Imp: SELECTIVITY: It is the ability to select the signal of a particular frequency & to reject the other frequencies.

Q-factor & Bandwidth:  $Q = \frac{f_r}{\Delta f}$  or  $Q = \frac{\omega_r}{\Delta \omega}$

$\therefore$  Q-factor  $\propto \frac{1}{\text{Bandwidth} (\Delta f)}$

If  $\Delta f$  is narrow  $\rightarrow$  Q-factor  $\rightarrow$  High

If  $\Delta f$  is broad  $\rightarrow$  Q-factor  $\rightarrow$  Low

For large values of 'Q', curve becomes flatter.

selectivity


selectivity

selectivity


selectivity

selectivity

selectivity

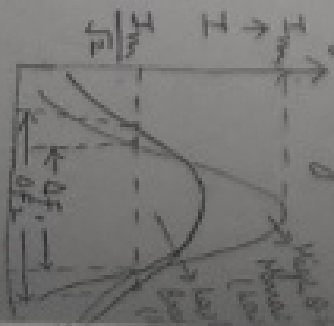

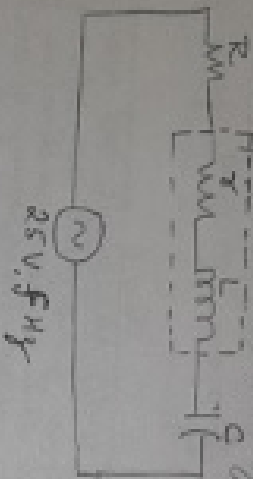Ques: A 20- $\Omega$  resistor is connected in series with an inductor and a capacitor, across a variable frequency AC supply. When the frequency is 400 Hz, the current is at its maximum value of 0.5 A & the potential difference across the capacitor is 150 V. Calculate the resistance & inductance of inductor. Also find



$$V_L = V_C = 150V$$

$$I_{max} = 0.5A \quad \{Z = R + jX\}$$

$$I_{max} = \frac{V}{Z}$$

$$0.5 = \frac{25}{20 + X}$$

$$X = 30\Omega$$

$$V_C = I_{max} \cdot X_C$$

$$150 = 0.5 \times \frac{1}{\omega C}$$

$$C = \frac{1}{\omega C} = \frac{1}{2\pi \times 400 \times 300}$$

$$V_L = I_{max} \cdot X_L$$

$$150 = 0.5 \times \omega L$$

$$L = \frac{1}{\omega L} = \frac{1}{2\pi \times 400 \times 150}$$

Ans: Calculate the power factor if  $V(t) = V_m \sin(\omega t - 45^\circ)$  and  $I(t) = I_m \sin(\omega t + 135^\circ)$ .

$$V(t) = \frac{V_m}{\sqrt{2}} \angle -45^\circ$$


$$I(t) = \frac{I_m}{\sqrt{2}} \angle 135^\circ$$

$$\phi = V \angle I = (-45^\circ + 135^\circ) = 90^\circ$$

$$\cos \phi = \cos(90^\circ) = 0$$
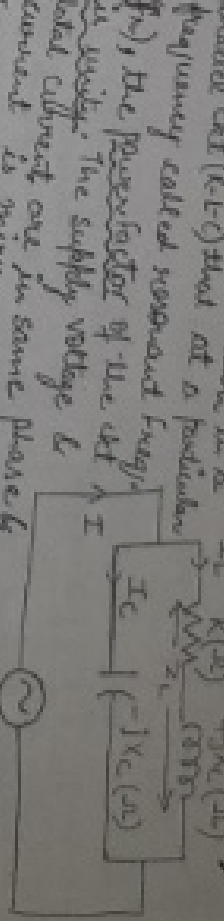
### RESONANCE IN PARALLEL R-L-C CIR

Consider in the condition in a parallel R-L-C circuit at a particular frequency called resonant frequency, the reactance of the circuit is zero. The supply voltage & current is maximum.



Impedance of inductive branch  $Z_L = \sqrt{R^2 + X_L^2}$

Impedance of capacitive branch  $Z_C = \sqrt{R^2 + X_C^2}$

Phasor Diagram:

At resonant frequency, the reactance of inductor is equal to the reactance of capacitor.

Total current  $I = I_L \cos \phi_L + I_C \cos \phi_C$

Power factor  $\cos \phi = \frac{R}{Z}$

Power factor  $\cos \phi = \frac{X_L}{Z}$

Power factor  $\cos \phi = \frac{X_C}{Z}$

Power factor  $\cos \phi = \frac{V}{Z}$

Power factor  $\cos \phi = \frac{I_C}{I}$

Power factor  $\cos \phi = \frac{I_L}{I}$

Power factor  $\cos \phi = \frac{V}{Z}$

Power factor  $\cos \phi = \frac{I_C}{I}$

If  $\frac{R^2}{L^2} \rightarrow$  neglected.

$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{Hz (For Ideal Case)}$$

### DYNAMIC IMPEDANCE:

(HKTU 2018-20)  
The impedance offered by the parallel ckt at resonance is called dynamic impedance of the ckt.

At resonance,

$$I = I_L \cos \phi_L$$

$$I = \frac{V}{Z_L} \cdot \frac{R}{Z_L}$$

$$I = \frac{V \cdot R}{Z_L^2}$$

$$I = \frac{V}{Z}$$

$$\frac{1}{R} \rightarrow Z_D \text{ (Dynamic Impedance)}$$

$$Z_D = \frac{L}{RC} \Omega$$

As  $I$  is minimum at resonance,  $Z_D$  is high.

Important Points :-

1) Impedance is max.  $Z_D = \frac{L}{RC} \Omega$

2) Current is minimum  $I = \frac{V}{Z_D}$

3) Power factor is unity ( $\cos \phi = 1$ )

4) Admittance is minimum

### APPLICATIONS:-

- 1) R-F Oscillations
- 2) Complex Communication ckt.
- 3) Impedance Transformation
- 4) In Filters.

### Q-FACTOR OF PARALLEL R-L-C CKT AT RESONANCE

CURRENT OR MAGNIFICATION

Q = Current in inductive/capacitive branch

$$Q = \frac{I_L}{I} = \frac{V/Z_L}{V/Z_D} = \frac{Z_D}{Z_L} = \frac{L}{R \sqrt{LC}}$$

$$Q = \frac{Z_D}{Z_L} = \frac{L}{R \sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Ques:- Why parallel ckt at resonance is called a rejector ckt?  
Ans:- In parallel resonance, at resonant frequency, current is minimum and impedance is maximum. If it is the signals of a particular frequency. Hence it is called a rejector ckt and is used in filters.

As  $f$  increases,  $Z_L = \sqrt{R^2 + X_L^2} \rightarrow$  inc. &  $\cos \phi_L = \frac{R}{Z_L} \rightarrow$  dec. so  $I = I_L \cos \phi_L \rightarrow$  Minimum  $I$  at  $f_r$ .

Ques: A series a-c circuit has resistance of  $15 \Omega$  & inductive reactance of  $10 \Omega$ . Cal. the value of 'C' which is connected across that series combination so that the power factor is unity.

Ans:  $R = 15 \Omega$ ,  $X_L = 10 \Omega$   
This is parallel Resonance with  $f_r = 50 \text{ Hz}$

$$X_L = 2\pi f_r L$$

$$L = \frac{10}{2\pi \cdot 50} = 0.03183 \text{ H}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$50 = \frac{1}{2\pi \cdot 0.03183} \sqrt{\frac{1}{LC} - \frac{15^2}{(0.03183)^2}}$$

$$C = 97.94 \mu\text{F}$$

### Comparison B/w Series and Parallel Resonance

| S. No. | Parameter           | Series Resonance                     | Parallel Resonance                   |
|--------|---------------------|--------------------------------------|--------------------------------------|
| 1)     | Circuit             | $\rightarrow$ R in series with C     | $\rightarrow$ R in parallel with C   |
| 2)     | Type of circuit     | Purely Resistive                     | Purely Resistive                     |
| 3)     | Power factor        | Unity                                | Unity                                |
| 4)     | Impedance           | Minimum $Z = R$                      | Maximum $Z = \frac{L}{RC}$           |
| 5)     | Frequency ( $f_r$ ) | $f_r = \frac{1}{2\pi\sqrt{LC}}$      | $f_r = \frac{1}{2\pi\sqrt{LC}}$      |
| 6)     | Current ( $I$ )     | Maximum $I = \frac{V}{R}$            | Minimum $I = \frac{V}{Z_D}$          |
| 7)     | Magnification       | Voltage Magnification                | Current Magnification                |
| 8)     | Quality factor (Q)  | $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$ | $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$ |


# AC PARALLEL CIRCUIT

A Parallel ckt is one in which two or more impedances are connected in parallel across the supply voltage.

$$\vec{I} = \vec{I}_1 + \vec{I}_2 + \vec{I}_3$$

$$\frac{\vec{V}}{Z} = \frac{\vec{V}}{Z_1} + \frac{\vec{V}}{Z_2} + \frac{\vec{V}}{Z_3}$$
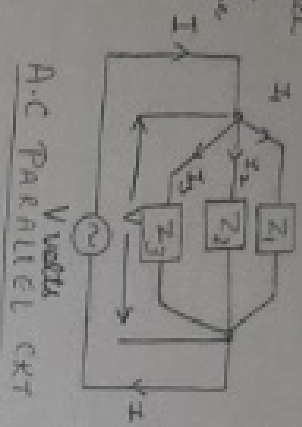
$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$



## TWO IMPEDANCES IN PARALLEL

If two impedances are in parallel and  $\vec{I}_T$  is the total current, then for calculating individual branch current, Apply Current Division Rule -

$$\vec{I}_1 = \vec{I}_T \times \frac{Z_2}{Z_1 + Z_2}$$

$$\vec{I}_2 = \vec{I}_T \times \frac{Z_1}{Z_1 + Z_2}$$

ADMITTANCE :- is defined as the reciprocal of Impedance.

$$Z = R + jX$$

Admittance (Y) =  $\frac{1}{Z}$  (Impedance)

$$Y = \frac{1}{Z} = \frac{1}{R + jX}$$

Rationalizing the above expression:-

$$Y = \frac{R - jX}{(R + jX)(R - jX)} = \frac{R - jX}{R^2 + X^2}$$

$$Y = \left( \frac{R}{R^2 + X^2} \right) - j \left( \frac{X}{R^2 + X^2} \right) = \frac{R}{Z^2} - j \frac{X}{Z^2}$$

$$\therefore Y = G - jB$$

where  $G$  = Conductance =  $\frac{R}{Z^2}$

$B$  = Susceptance =  $\frac{X}{Z^2}$

In Polar form,  $Y = G + jB = |Y| \angle \phi$  Where  $\phi = \tan^{-1} \frac{B}{G}$

Ex-10.

Ques:- The parallel circuit is connected across a single phase 100V, 50 Hz A.C. supply. Calculate :-

- 1) The branch currents
- 2) The total current
- 3) Supply Power factor
- (4) Active Power, Reactive Power & Total Power of the ckt.
- (5) Power dissipated by each branch.

1)  $Z_1 = (8 + j6) \Omega = 10 \angle 36.86^\circ \Omega$

$$\vec{I}_1 = \frac{\vec{V}}{Z_1} = \frac{100 \angle 0^\circ}{10 \angle 36.86^\circ}$$

$$\vec{I}_1 = 10 \angle -36.86^\circ \text{ Amp}$$

$$\vec{I}_2 = \frac{\vec{V}}{Z_2}$$

$$Z_2 = (6 - j8) \Omega$$

$$Z_2 = 10 \angle -53.13^\circ \Omega$$

$$\therefore \vec{I}_2 = \frac{100 \angle 0^\circ}{10 \angle -53.13^\circ}$$

$$\vec{I}_2 = 10 \angle 53.13^\circ \text{ Amp}$$

(ii) Total current  $\vec{I} = \vec{I}_1 + \vec{I}_2$

$$\vec{I} = 10 \angle -36.86^\circ + 10 \angle 53.13^\circ$$


$$= (8 - j6) + (6 + j8)$$

$$\vec{I} = 14 + j2 \text{ Amp}$$

$$\vec{I} = 14.14 \angle 8.13^\circ \text{ Amp}$$

(iii) Power factor (cos  $\phi$ ) =  $\cos(8.13^\circ)$

$$\cos \phi = 0.989 \text{ (Leading)}$$

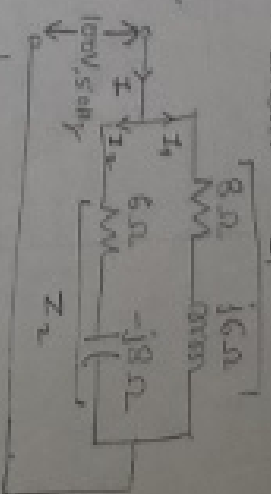

(iv) Active Power (P) =  $V_{rms} I_{rms} \cos \phi$

$$P = 100 \times 14.14 \times 0.989$$

$$P = 1399.71 \text{ watt}$$

Reactive Power (Q) =  $V_{rms} I_{rms} \sin \phi$

$$Q = 100 \times 14.14 \times \sin(8.13^\circ)$$

$$Q = 199.96 \text{ VAR}$$

Total Power (S) =  $V_{rms} \times I_{rms}$

$$S = 100 \times 14.14$$

$$S = 1414 \text{ VA}$$

(v) Power dissipated by branch

$$P_1 = I_1^2 R_1$$

$$P_1 = (10)^2 \times 8$$

$$P_1 = 800 \text{ watt}$$

$$P_2 = I_2^2 R_2$$

$$P_2 = (10)^2 \times 6$$

$$P_2 = 600 \text{ watt}$$

## POWER FACTOR IMPROVEMENT (AKTU 13-20, 16-17, 15-16, 13-14)

What is Power factor? What are the disadvantages and causes of low Power factor. Explain any one method to improve Power factor.

(AKTU 2016-17, 15-16, 13-14)

Def<sup>n</sup> Power Factor :-

$$\cos \phi = \frac{\text{Active Power}}{\text{Apparent Power}} = \frac{VI \cos \phi}{VI}$$

$$\text{also } \cos \phi = \frac{P}{VI}$$

$$\cos \phi >$$

~~Active Power~~  
~~Apparent Power~~

\* It shows that how much Percentage of Total Power is consumed by the ckt.  
It's a practical measure of the efficiency of Power distribution system.

$$P = VI \cos \phi \text{ watt}$$

or  $I = \frac{P}{V \cos \phi}$  as  $P \& V$  are constant. So  $I \propto \frac{1}{\cos \phi}$   
If P.F. is low,  $I$  is very high & vice versa.

Disadvantages of low Power factor :-

\* Large generators and transformers are required to deliver same load but at a low Power factor.

\* More conductor material is required for transmission lines due to large current.

\* Due to high current, more Cu loss occurs at low Power factor.

\* Low lagging Power factor results in large voltage drop in transformers, generators, & lines which results in poor regulation.

Causes of low Power factor :-

\* All a.c. motors and transformers operate at lagging Power factor. Power factor decreases with decrease in load.

\* Industrial heating furnaces such as arc and induction furnaces operate on very low lagging Power factor.

Power factor can be improved by :-

- \* Using induction motors with phase advance.
- \* Connecting the static capacitors in parallel with the equipment operating at lagging Power factor.
- \* By using synchronous condensers, self starting capacitor connected across the supply.

Power factor can be improved by shunt capacitor.



For inductive load,  $I_L$  lags  $V$  by  $\phi_L$ .

Capacitor is connected in parallel with inductor.  $I_c$  leads  $V$  by  $90^\circ$ .

$$\text{Current } \vec{I} = \vec{I}_L + \vec{I}_c$$

$\therefore I$  lags  $V$  by  $\phi$

$$\phi < \phi_L$$

$$\cos \phi > \cos \phi_L$$

Hence, Power factor is improved.



## THREE PHASE T.Y.C. CIRCUIT

### ADVANTAGES OF THREE PHASE SYSTEM OVER SINGLE PHASE SYSTEM :-

- \* The rating of a machine increase with increase in number of phases.
- \* Power Factor of a 1 $\phi$  motor is lower than that of a three-phase motor of same rating.
- \* Three-phase motor has more output (> 1.5 times) than single phase motor.
- \* 3 $\phi$  system is more reliable & capable than single phase system.
- \* 3 $\phi$  system having higher efficiency as compared to 1 $\phi$  system.

### SOME BASIC TERMS RELATED TO 3 $\phi$ AC SYSTEM :-

- 1) Phase Voltage ( $V_p$ ): It is defined as the voltage across either phase winding or load terminal.  
 $V_R, V_Y$  &  $V_B$  are the phase voltages across R, Y & B phase of Star & Delta connection respectively.
  - 2) Line Voltage ( $V_L$ ): It is defined as the voltage across any two line terminals.  
 $V_{RY}, V_{YB}$  &  $V_{BR}$  are the line voltages measured b/w R-Y, Y-B & B-R terminal for Star & Delta connections.
  - 3) Phase Current ( $I_p$ ): It is defined as the current flowing through each phase winding or load.
  - 4) Line Current ( $I_L$ ): It is defined as the current flowing through each line wire.
- Phase Sequence :- The order in which three coil's EMF currents attain their maximum values is often the order is called Phase sequence.

### V. Example

B. Tech I Year [Subject Name: Electrical Engineering]

Ques: A 3 $\phi$  voltage source has a phase voltage of 120V ac. It supplies star connected load having impedance (30+j40)  $\Omega$  per phase. Calculate:-

- 1) line voltage (b) line current (c) Power factor (d) total 3 $\phi$  Power supplied to the load. (A.K.T.V 2013-14, 14-15)
- 2)  $\cos \phi$  for Star or connected system?

(a)  $V_L = \sqrt{3} V_p$  (b)  $I_L = I_p$

(c)  $V_L = \sqrt{3} \times 120$   $I_p = \frac{V_p}{Z_p} = \frac{120 \angle 0^\circ}{60 \angle 53.13^\circ} = 2 \angle -53.13^\circ \text{ A}$

$V_L = 207.8 \text{ V}$   $I_L = 2.078 \text{ A}$

(d)  $\cos \phi = \cos(-53.13^\circ)$   $I_p = I_L = 2 \angle -53.13^\circ \text{ Amp}$

$\cos \phi = 0.6$  (lagging)  $P = \sqrt{3} V_L I_L \cos \phi \text{ watt}$

$P = \sqrt{3} \times 207.8 \times 2 \times 0.6$

Ans: A  $\Delta$ -connected load is supplied from 400V 3 $\phi$  mains. The line current is 20A, and the power taken by the load is 10kW. Find:-

- 1) Impedance in each branch (ii) Power factor of the load (iii) line current & power consumed if same load is connected in star.

soln  $V_L = 400 \text{ V}$ ,  $I_L = 20 \text{ A}$ ,  $P = 10 \text{ kW}$

$P = \sqrt{3} V_L I_L \cos \phi$  i.e.  $10 \times 10^3 = \sqrt{3} \times 400 \times 20 \times \cos \phi$

$\therefore \cos \phi = 0.721$  i.e.  $\phi = 43.8^\circ$

1)  $V_p = V_L = 400 \text{ V}$  (ii)  $Z_p = \frac{V_p}{I_p}$

$I_p = \frac{I_L}{\sqrt{3}} = \frac{20}{\sqrt{3}} = 11.54 \text{ Amp}$   $P_p = \frac{400^2}{11.54} = 34.64 \text{ W}$

$$(2) \cos \phi = \cos \phi_{43.8^\circ}$$

$$[\cos 43.8^\circ = .721] \text{ (lagging)}$$

(3) for star connected system

$$V_L = \sqrt{3} V_P$$

$$\& I_L = I_P$$

$$\therefore V_P = \frac{V_L}{\sqrt{3}} = 230.94V$$

$$I_P = \frac{V_P}{Z_P} = \frac{230.94}{34.64}$$

$$I_P = 6.667 \text{ Amp} = I_L$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 400 \times 6.667 \times .721$$

$$P = 3.33 \text{ KW}$$

Ques A balanced 3 $\phi$  star-connected load of 18KW taking a line current of 60 amp when connected across a 3 $\phi$  440V, 50Hz supply. Find the values and nature of load & power factor of the load. AKTU (2015-16)

Sol<sup>n</sup> for  $\Delta$  connection.

$$V_L = \sqrt{3} V_P \& I_L = I_P$$

$$V_L = 440V, P = 18 \times 10^3 \text{ watt}$$

$$I_L = 60 \text{ Amp}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$18 \times 10^3 = \sqrt{3} \times 440 \times 60 \cos \phi$$

$$\cos \phi = .39$$

$$\text{or } P = -66.81$$

$$V_P = \frac{V_L}{\sqrt{3}} = \frac{440}{\sqrt{3}} = 254.03 \text{ Volt}$$

$$I_L = I_P = 60 \text{ Amp}$$

$$Z_P = \frac{V_P}{I_P} = \frac{254.03}{60}$$

$$Z_P = 4.23 \Omega$$

$$R_P = Z_P \cos \phi$$

$$R_P = 1.66 \Omega$$

$$X_P = Z_P \sin \phi$$

$$X_P = 4.23 \sin (66.81^\circ)$$

$$X_P = 3.89 \Omega$$

$$\text{or } X_P = \frac{1}{\omega C}$$

$$\omega C = .81 \text{ mF}$$


5 Year's

University Paper Questions

(AKTU Question Bank)

mt

| 3 Years University Examination Questions |                                                                                                                                                                                                                                                |                         | Unit-2 |      |
|------------------------------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------|--------|------|
| No                                       | Questions                                                                                                                                                                                                                                      | Session                 | Max.   | Ans. |
| 1                                        | Write a note on: Amplitude, mechanical equivalent angular velocity.                                                                                                                                                                            | (2017-18)<br>18/05/2018 | 11     |      |
| 2                                        | The equation of an alternating current is $i = 10\sqrt{2} \sin 314t$ . What will be r.m.s. value of current and frequency?                                                                                                                     | (2018-19)<br>18/05/2019 | 11     |      |
| 3                                        | The equation of an alternating current $i = 42.42 \sin 628 t$ . Determine (i) instantaneous (ii) frequency (iii) rms value (iv) average value (v) form factor $w(t)$ .                                                                         | (2017-18)<br>18/05/2018 | 11,12  |      |
| 4                                        | Find the r.m.s. value, average value and form factor of the given waveforms.                                                                                                                                                                   | (2017-18)<br>0000       | 11,12  |      |
| 5                                        | Derive expression for average value and r.m.s. value of half wave rectifier voltage output.                                                                                                                                                    | (2020-21)<br>0000       | 12,13  |      |
| 6                                        | Determine the form factor of AC current $i = 200 \sin (1.57 t + \pi/6)$ .                                                                                                                                                                      | (2019-20)<br>0000       | 12,13  |      |
| 7                                        | Derive expressions for average value and r.m.s. value of a sinusoidal varying AC voltage.                                                                                                                                                      | (2017-18)<br>28/05/2018 | 12,13  |      |
| 8                                        | Explain the form factor and peak factor.                                                                                                                                                                                                       | (2017-18)<br>18/05/2018 | 12,13  |      |
| 9                                        | Calculate average value, rms value, form factor and peak factor of the following waveform shown in figure.                                                                                                                                     | (2017-18)<br>0000       | 12,13  |      |
| 10                                       | The instantaneous values of two alternating voltages are represented by $V_1 = 60 \sin \theta$ and $V_2 = 50 \sin (\theta - \pi/3)$ . Derive expression for the instantaneous values of (i) the sum and (ii) the difference of these voltages. | (2018-19)<br>0000       | 14     |      |
| 11                                       | The two voltage waves are given:<br>$V_1 = 150 \sin (\omega t + 45^\circ)$ and $V_2 = 75 \sin (\omega t - 15^\circ)$<br>What voltage wave is leading with other and what will be the phase angle between $V_1$ and $V_2$ .                     | (2018-19)<br>0000       | 14     |      |
| 12                                       | Draw the phasor diagram for the following voltages. Calculate the resultant voltage. Also find the r.m.s. voltage.<br>$V_1 = 100 \sin 500t$<br>$V_2 = 200 \sin (500t + \pi/3)$<br>$V_3 = 150 \sin (500t - \pi/4)$                              | (2018-19)<br>0000       | 14     |      |

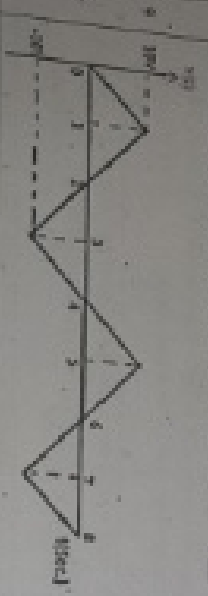

|    |                                                                                                                                                                                                                                                                                                                                                             |                         |       |  |
|----|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------|-------|--|
| 13 | Draw a phasor diagram showing the following voltages:<br>$V_1 = 500 \sin 500t$<br>$V_2 = 250 \sin (500t + 45^\circ)$<br>$V_3 = 500 \cos t$                                                                                                                                                                                                                  | (2017-18)<br>0000       | 14    |  |
| 14 | Find rms value of resultant voltage<br>What is phase angle difference between the voltage and current phasor in a purely capacitive circuit?                                                                                                                                                                                                                | (2018-19)<br>18/05/2018 | 15    |  |
| 15 | Derive the expressions for the average power in a single phase purely resistive circuit. Also draw the phasor diagram and waveform diagram for this circuit.                                                                                                                                                                                                | (2018-19)<br>18/05/2018 | 15    |  |
| 16 | A 120V, 200W lamp is to be connected to 220 volt, 50Hz supply. In order that lamp should operate on correct voltage, calculate the value of (i) non inductive reactance (ii) Pure Inductance.                                                                                                                                                               | (2017-18)<br>0000       | 16    |  |
| 17 | Acinductor-inductor-capacitor-resistor series across a 200V, 50 Hz supply. The voltage across each is 120V, 120V and 240V respectively. If the steady current is 0.5 A, calculate:<br>1.) The resistance and inductance of the coil<br>2.) The power dissipated in the coil<br>3.) The power factor of the circuit.<br>4.) The power factor of the circuit. | (2018-19)<br>0000       | 16    |  |
| 18 | A resistance and inductance are connected in series with voltage $v = 283 \sin 314t$ . The current opposition is found to be $i = 4 \sin (314t - 67^\circ)$ . Find the value of resistance, inductance and power factor.                                                                                                                                    | (2018-19)<br>18/05/2018 | 16    |  |
| 19 | If load draws a current of 10A at 0.8 p.f. lagging when connected to 100 V supply, calculate the values of real, reactive and apparent power. And also find the resistance of load.                                                                                                                                                                         | (2020-21)<br>0000       | 16,17 |  |
| 20 | What is the power factor of a circuit having impedance of $2+j4$ ohms.                                                                                                                                                                                                                                                                                      | (2017-18)<br>0000       | 16,17 |  |
| 21 | A non inductive resistance of 10 ohm is connected in series with an inductive coil across 200 V, 50 Hz ac supply. The current flows by the series combination is 10 Amp. The resistance of coil is 2 ohms. Determine:<br>i) Inductance of the coil ii) Power factor iii) Voltage across the coil.                                                           | (2017-18)<br>0000       | 16,17 |  |
| 22 | Derive expressions for impedance, current and power factor for an R-L-C series circuit when supplied with AC voltage. Draw also the vector diagram.                                                                                                                                                                                                         | (2017-18)<br>18/05/2018 | 17    |  |
| 23 | A 45 mill inductive coil has a resistance of 10 ohms. How much current will it draw, if connected across 100 V, 50 Hz source? Also determine the value of capacitance that must be connected across the coil to make the power factor of the circuit to be unity.                                                                                           | (2018-19)<br>18/05/2018 | 17    |  |
| 24 | A series ac circuit has a resistance of 150 and inductive reactance of 10 Ohm. Calculate the value of a capacitor which is connected across this series combination so that system has unity power factor. The frequency of ac supply is 50Hz.                                                                                                              | (2018-19)<br>0000       | 17    |  |
| 25 | What do you mean by apparent power, active power and reactive power?                                                                                                                                                                                                                                                                                        | (2018-19)<br>18/05/2018 | 17    |  |
| 26 | A 40 V d.c. source has internal resistance of 2 ohm and supplies a resistive load. What can be maximum power drawn by the load?                                                                                                                                                                                                                             | (2018-19)<br>18/05/2018 | 17    |  |
| 27 | A coil having a resistance of 30 ohm and inductance of 0.05 H is connected in series with a capacitor of 100 $\mu$ F. The whole circuit has                                                                                                                                                                                                                 | (2018-19)<br>18/05/2018 | 17    |  |

**B. Tech I Year [Subject Name: Fund. Of Electrical Engineering]**

|    |                                                                                                                                                                                                                                                                                                                                                         |               |    |
|----|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------|----|
|    | been connected to a single phase 230 V, 50 Hz supply. Calculate impedance, current, power factor, power and apparent power of the circuit.                                                                                                                                                                                                              |               |    |
| 38 | A series RLC circuit is composed of 10 $\Omega$ resistance, 0.1 H inductance and 50 $\mu$ F capacitance. A voltage $v(t) = 241.4 \cos(100\pi t)$ V is impressed upon the circuit. Determine (i) the expression for instantaneous current, (ii) the voltage drops $V_R$ , $V_L$ and $V_C$ (iii) draw the phasor diagram using all the voltage relations. | (2014-15) 000 | 17 |
| 39 | Derive an expression of resonance frequency in series resonance circuit. If the bandwidth of a resonant circuit is 10 kHz and the lower half power frequency is 120 kHz, find out the value of the upper half power frequency and the quality factor of the circuit.                                                                                    | (2014-15) 000 | 18 |
| 40 | Derive an expression of resonance frequency for series RLC circuit. A series circuit consists of a resistance of 15 $\Omega$ , and inductance of 50 mH and a variable capacitance is series across a 100V, 50Hz supply. Calculate:<br>(i) The value of capacitance to produce resonance.<br>(ii) Voltage across the capacitance.<br>(iii) Q-factor      | (2014-15) 000 | 19 |
| 41 | Why series resonant circuit is known as acceptor circuit & parallel resonant circuit as rejector circuit?                                                                                                                                                                                                                                               | (2013-14) 000 | 18 |
| 42 | Explain series resonance in RLC circuit. What are the bandwidth and quality factor of the circuit? Derive expressions for lower and upper half power frequencies for a series RLC circuit.                                                                                                                                                              | (2013-14) 000 | 19 |
| 43 | Explain resonance in a series RLC circuit with the help of impedance vs frequency diagram and derive an expression for resonant frequency. Write properties of series resonance circuit.                                                                                                                                                                | (2013-14) 000 | 19 |
| 44 | Derive resonance conditions in series circuit. Also derive the expression for Bandwidth.                                                                                                                                                                                                                                                                | (2013-14) 000 | 18 |
| 45 | Derive the condition for resonance in series RLC circuit. What are the different applications of resonance?                                                                                                                                                                                                                                             | (2013-14) 000 | 18 |
| 46 | A series circuit has $R = 100 \Omega$ , $L = 0.02$ H and $C = 2 \mu$ F. Calculate Q-factor of the circuit.                                                                                                                                                                                                                                              | (2013-14) 000 | 19 |
| 47 | Derive the expression of bandwidth of a series RLC circuit. Explain the relationship between bandwidth and quality factor.                                                                                                                                                                                                                              | (2013-14) 000 | 19 |
| 48 | A series circuit has $R = 10 \Omega$ , $L = 0.05$ H and $C = 10 \mu$ F. Calculate Q-factor of the circuit.                                                                                                                                                                                                                                              | (2013-14) 000 | 19 |
| 49 | Explain the concepts of bandwidth and quality factor for series RLC circuit. Derive the expressions.                                                                                                                                                                                                                                                    | (2013-14) 000 | 19 |
| 50 | Derive the quality factor Q of the series R-L-C circuit at resonance. Define the bandwidth for the same.                                                                                                                                                                                                                                                | (2013-14) 000 | 19 |
| 51 | Explain the term "Dynamic impedance" in AC circuits. OR<br>Derive mathematically dynamic impedance ( $Z_d$ ) offered by RLC parallel                                                                                                                                                                                                                    | (2013-14) 000 | 20 |

**B. Tech I Year [Subject Name: Fund. Of Electrical Engineering]**

|    |                                                                                                                                                                                                                                                                                                                                   |               |    |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------|----|
|    | circuit under resonance. Also, draw its phasor diagram.                                                                                                                                                                                                                                                                           | (2013-14) 000 |    |
| 42 | Derive the expression for resonant frequency & quality factor for an AC circuit under the condition of parallel resonance.                                                                                                                                                                                                        | (2013-14) 000 | 19 |
| 43 | Explain parallel resonance. A circuit of a resistance of 20 $\Omega$ , and inductance of 0.1 H and a variable capacitance in series across a 230 V, 50 Hz supply. Calculate:<br>(i) The value of capacitance to produce resonance<br>(ii) The voltage across the capacitance and inductance<br>(iii) The Q-factor of the circuit. | (2013-14) 000 | 19 |
| 44 | Derive power factor. Discuss reasons for poor power factor. How can power factor be improved?                                                                                                                                                                                                                                     | (2013-14) 000 | 19 |
| 45 | A balanced star connected load of (8-j6) $\Omega$ per phase is connected to a 3-phase, 400V supply. Find the line current, power factor, power and total watt-ampere.                                                                                                                                                             | (2013-14) 000 | 19 |
| 46 | Derive the relation between line current & phase current in case of three phase delta connected balanced load. Three identical coils of resistance 8 $\Omega$ and inductive reactance 6 $\Omega$ are connected in delta across 400V mains. Determine power, power factor and line current. Draw phasor diagram.                   | (2013-14) 000 | 19 |
| 47 | A balanced star connected load of (8-j6) $\Omega$ per phase is connected to a 3-phase, 400V supply. Find the line current, power factor, power and total watt-ampere.                                                                                                                                                             | (2013-14) 000 | 19 |
| 48 | Derive the relationship between line current and phase current for delta connected 3-phase load when supplied from 3-phase balanced supply.                                                                                                                                                                                       | (2013-14) 000 | 19 |
| 49 | A balanced star connected load of (8 + j6) $\Omega$ per phase is connected to a 3-phase 400V supply. Find the line current, power factor, 3-phase power and 3-phase watt-ampere. Also draw the phasor diagram.                                                                                                                    | (2013-14) 000 | 19 |
| 50 | Three similar coils each having a resistance of 10 $\Omega$ and an inductance of 0.1 H are connected in delta. The line voltage is 400V, 50 Hz. Calculate: phase current, line current, power factor, total power in the circuit.                                                                                                 | (2013-14) 000 | 19 |
| 51 | Obtain the relation between line & phase voltages in balanced star connected load system. Also draw its phasor diagram. A 3-phase, star connected balanced load is supplied by 400 V, 50 Hz. The load takes a line current of 100 A & power 20 kW. Calculate power factor of load and Resistance & Inductance per phase.          | (2013-14) 000 | 19 |
| 52 | A balanced star connected load of (8-j6) $\Omega$ per phase is connected to a 3-phase 400V supply. Find the phase current, line current, power factor, power, reactive power and total power. Also draw the phasor diagram.                                                                                                       | (2013-14) 000 | 19 |
| 53 | A three-phase load consists of three similar inductors, each of inductance 0.3 H. The supply is 415 V, 50 Hz.                                                                                                                                                                                                                     | (2013-14) 000 | 19 |

|                      |  |
|----------------------|--|
| 91, 17-14-15, 20, 21 |  |
| 14-20, 21            |  |
| 20, 21               |  |
| 19-20, 21            |  |
| 15-22                |  |
| 13-14                |  |
| 21, 22               |  |
| 19-20, 21            |  |
| 17, 15-14            |  |
| 14                   |  |
| 2017-2018            |  |
| 2017-2018            |  |
| 2016-2017            |  |
| 2015-2016            |  |
| 1514-1515            |  |
| 15                   |  |